

# **BE LAB TASK # 12/13**

**Name: Shahmeer khan.**

**Class ID: 106293.**

**Student ID: 12113.**

**Topic: Non-Inverting  
Voltage Amplifier.**

## **Objectives:**

In this exercise, the performance of the non-inverting voltage amplifier will be examined. The investigation will include the effect of feedback resistors on setting voltage gain, stability of gain with differing op amps, and input impedance.

## **Task (According to Sir):**

### **1) Calculations From Voltage 0.3 V:**

- **Theoretical Av:**

- Since Formula:
- $A_v = 1 + R_f / R_{in}$ .

$$A_v = 1 + 2k / 1k = 3$$

$$A_v = 1 + 4.7k / 1k = 5.7$$

$$A_v = 1 + 10k / 1k = 11$$

$$A_v = 1 + 22k / 1k = 23$$

$$A_v = 1 + 33k / 1k = 34$$

$$A_v = 1 + 47k / 1k = 48$$

- **Experimental Av:**

- Since Formula:
- $A_v = V_{out} / V_{in}$

$$A_v = 0.8999973 \text{ V} / 0.3 \text{ V} = 2.999991$$

$$A_v = 1.71 \text{ V} / 0.3 \text{ V} = 5.7$$

$$A_v = 3.3 \text{ V} / 0.3 \text{ V} = 11$$

$$A_v = 6.898 \text{ V} / 0.3 \text{ V} = 22.99$$

$$A_v = 10.197 \text{ V} / 0.3 \text{ V} = 33.99$$

$$A_v = 14.393 \text{ V} / 0.3 \text{ V} = 47.97$$

### • Deviation:

$$A_v (\text{Theoretical}) - A_v (\text{Experimental}) \times 100 / A_v (\text{Theoretical})$$

$$3 - 2.999991 \times 100 / 3 = 0.003$$

$$5.7 - 5.7 \times 100 / 5.7 = 0$$

$$11 - 11 \times 100 / 11 = 0$$

$$23 - 22.99 \times 100 / 23 = 0.04$$


$$34 - 33.99 \times 100 / 34 = 0.02$$

$$48 - 47.97 \times 100 / 48 = 0.06$$

RF	THEORETICAL AV	V OUT	EXPERIMENTAL AV	% DEVIATION
2 k	3	899.973 m Vpk	2.99	0.33


<b>4.7k</b>	5.7	1.71 Vpk	5.7	0
<b>10k</b>	11	3.3 Vpk	11	0
<b>22K</b>	23	6.898 Vpk	22.99	0.04
<b>33k</b>	34	10.197 Vpk	33.99	0.02
<b>47k</b>	48	14.393 Vpk	47.97	0.06

### Screen-shots:

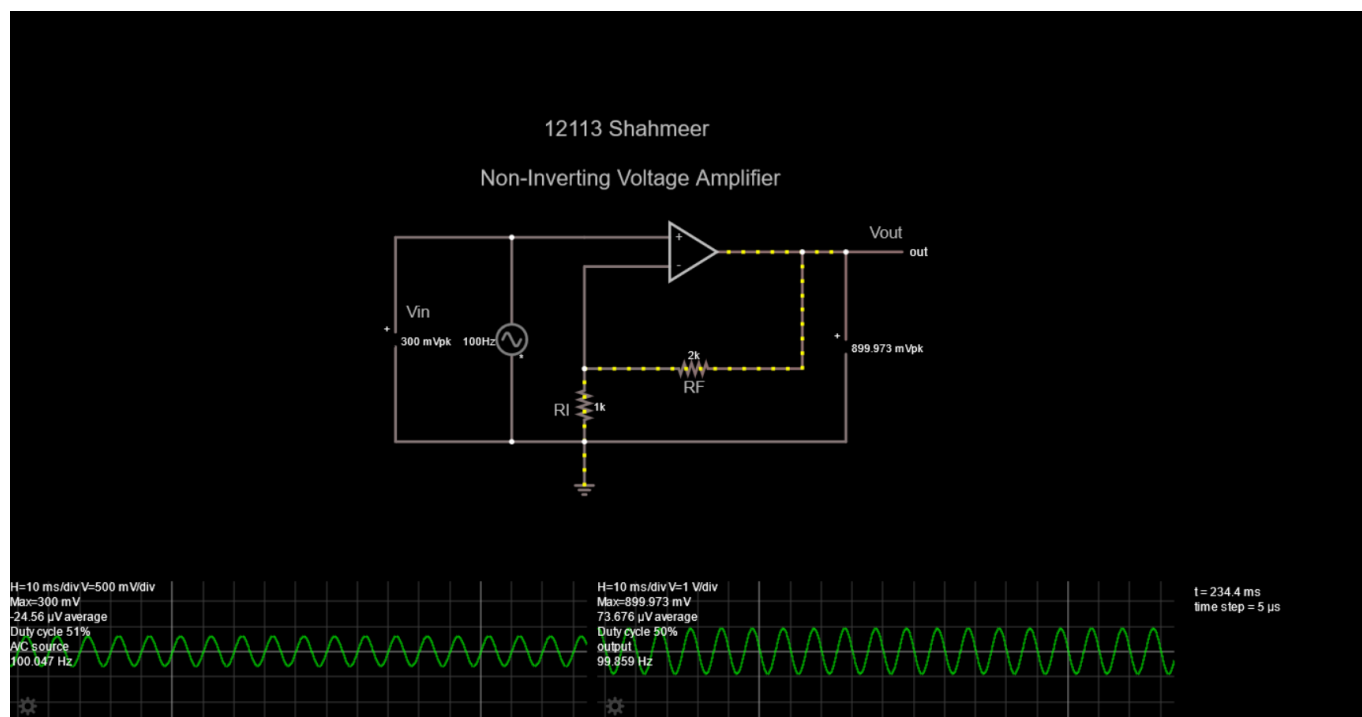


12113 Shahmeer


### Non-Inverting Voltage Amplifier

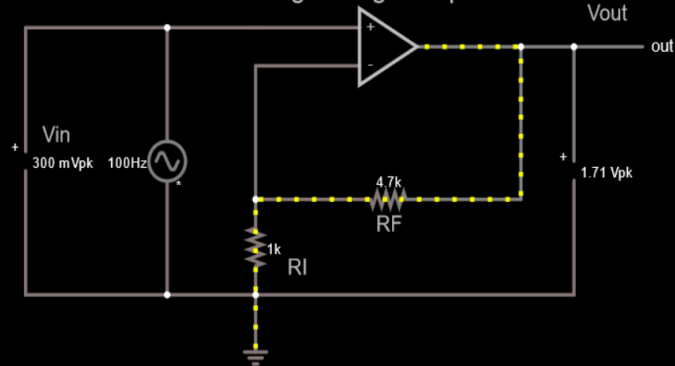

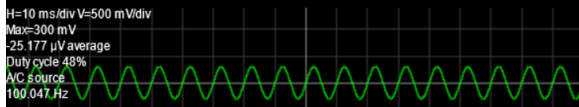H=10 ms/div V=500 mV/div  
Max=300 mV  
-25.177  $\mu$ V average  
Duty cycle 48%  
A/C source  
100.047 Hz



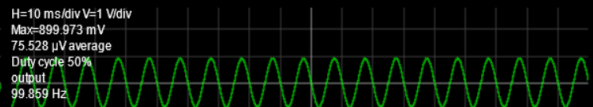
H=10 ms/div V=1 V/div  
Max=899.973 mV  
75.528  $\mu$ V average  
Duty cycle 50%  
output  
99.859 Hz




output  
V = 129.606 mV

12113 Shahmeer


### Non-Inverting Voltage Amplifier

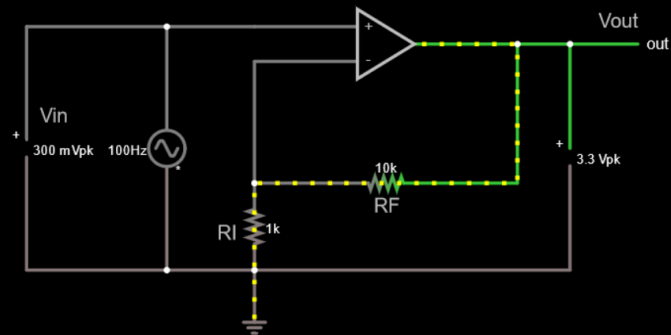

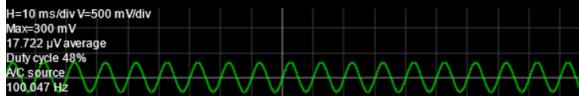H=10 ms/div V=500 mV/div  
Max=300 mV  
17.722  $\mu$ V average  
Duty cycle 48%  
A/C source  
100.047 Hz



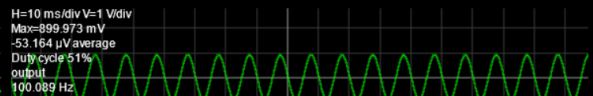
H=10 ms/div V=1 V/div  
Max=899.973 mV  
-53.164  $\mu$ V average  
Duty cycle 51%  
output  
100.089 Hz



output  
V = 899.689 mV

12113 Shahmeer

### Non-Inverting Voltage Amplifier

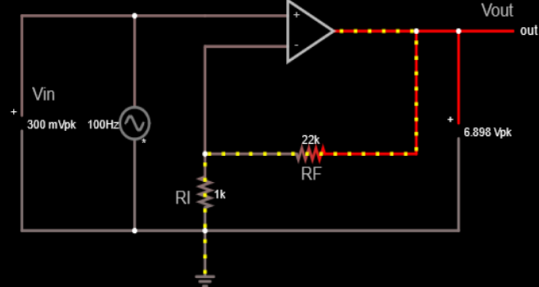


H=10 ms/div V=500 mV/div  
Max=300 mV  
33.742  $\mu$ V average  
Duty cycle 51%  
V/C source  
100.089 Hz

H=10 ms/div V=1 V/div  
Max=899.973 mV  
101.222  $\mu$ V average  
Duty cycle 50%  
output  
99.859 Hz

output  
V= -753.753 mV

12113 Shahmeer


### Non-Inverting Voltage Amplifier

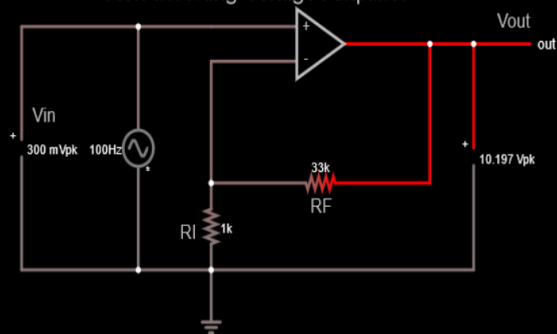

H=10 ms/div V=500 mV/div  
Max=300 mV  
25.262  $\mu$ V average  
Duty cycle 48%  
V/C source  
100.047 Hz

H=10 ms/div V=1 V/div  
Max=899.973 mV  
-75.784  $\mu$ V average  
Duty cycle 51%  
output  
100.047 Hz

output  
V= -665.648 mV

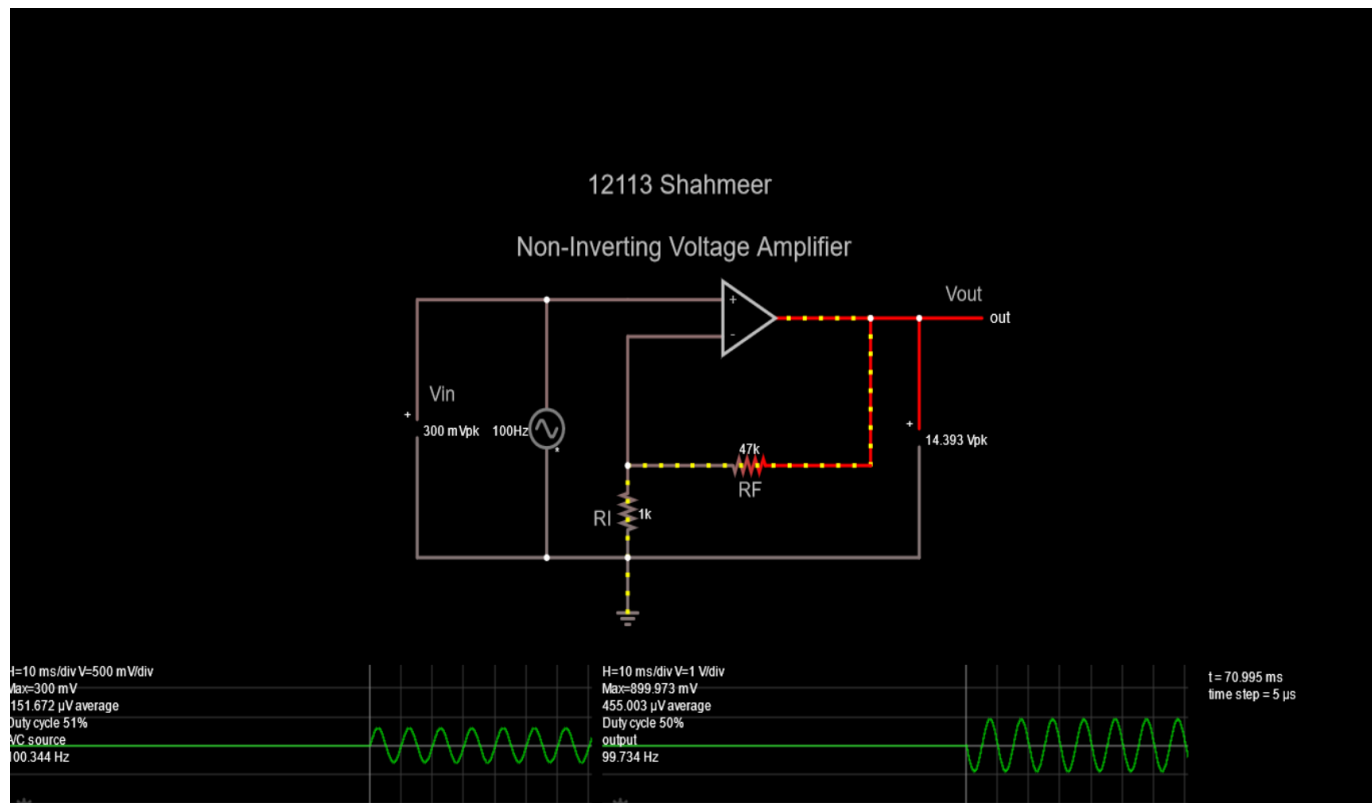

**Link:**

<https://tinyurl.com/yzg2ful6>

## **2) Calculations From Voltage 5 V:**

### **• Theoretical $A_v$ :**

#### **• Since Formula:**

#### **• $A_v = 1 + R_f / R_{in}$ .**

$$A_v = 1 + 2k / 1k = 3$$

$$A_v = 1 + 4.7k / 1k = 5.7$$

$$A_v = 1 + 10k / 1k = 11$$

$$A_v = 1 + 22k / 1k = 23$$

$$A_v = 1 + 33k / 1k = 34$$

$$A_v = 1 + 47k / 1k = 48$$

- **Experimental  $A_v$ :**

- **Since Formula:**

- **$A_v = V_{out} / V_{in}$**

$$A_v = 15V / 5V = 3$$

$$A_v = 15.043 / 5V = 3.0086$$

$$A_v = 15.011V / 5V = 3.0022$$

$$A_v = 15V / 5V = 3$$

$$A_v = 15V / 5V = 3$$

$$A_v = 15.063 / 5V = 3.0126$$

- **Deviation:**

$$AV \text{ (Theoretical)} - AV \text{ (Experimental)} \times 100 / AV \text{ (Theoretical)}$$

$$3 - 3 \times 100 / 3 = 0$$

$$5.7 - 3.0086 \times 100 / 5.7 = 47.21$$

$$11 - 3.0022 \times 100 / 11 = 72.70$$

$$23 - 3 \times 100 / 23 = 86.95$$


$$34 - 3 \times 100 / 34 = 91.17$$

$$48 - 3.0126 / 48 = 93.72$$




RF	Theoretical AV	V out	Experimental AV	Deviation %
2k	3	15 Vpk	3	0
4.7k	5.7	15.043 Vpk	3.0086	47.21
10k	11	15.011 Vpk	3.002	72.70
22k	23	15 Vpk	3	86.95
33k	34	15 Vpk	3	91.17
47k	48	15.062 Vpk	3.012	93.72

### Screen-shots:

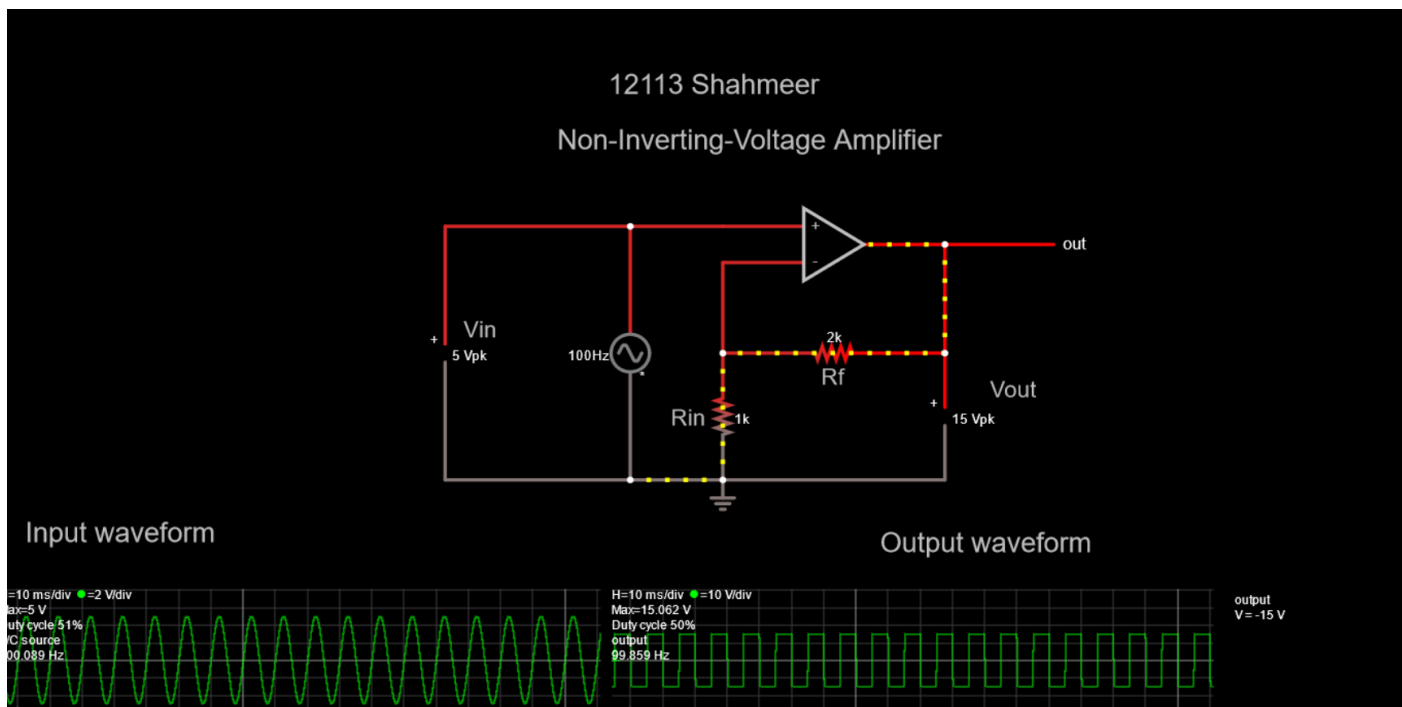


12113 Shahmeer

### Non-Inverting-Voltage Amplifier

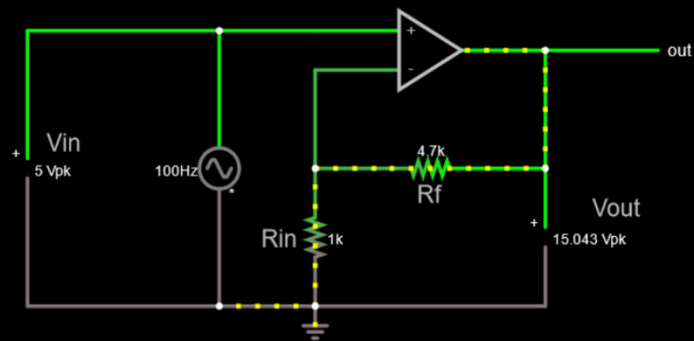

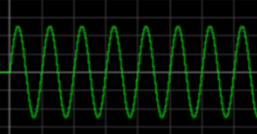H=10 ms/div ●=2 V/div  
Max=5 V  
Duty cycle 51%  
A/C source  
100.344 Hz




H=10 ms/div ●=10 V/div  
Max=15.062 V  
Duty cycle 48%  
output  
99.886 Hz




output  
V= 15 V

12113 Shahmeer


### Non-Inverting-Voltage Amplifier

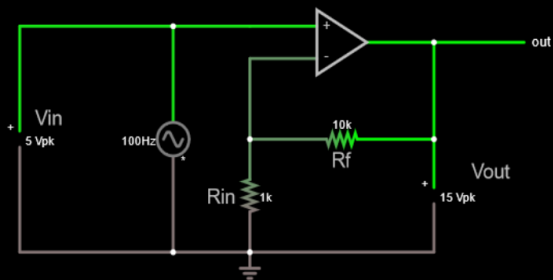

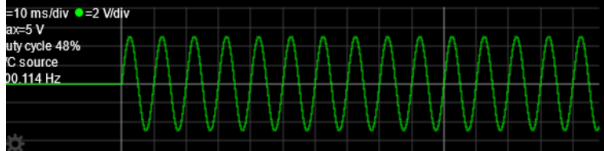H=10 ms/div ●=2 V/div  
Max=5 V  
Duty cycle 48%  
A/C source  
100.114 Hz



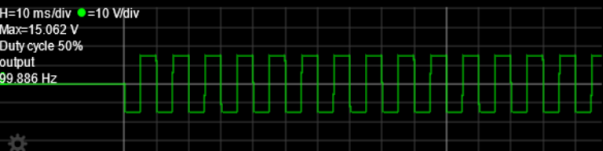
H=10 ms/div ●=10 V/div  
Max=15.062 V  
Duty cycle 50%  
output  
99.886 Hz




t = 148.165 ms  
time step = 5  $\mu$ s

12113 Shahmeer


### Non-Inverting-Voltage Amplifier

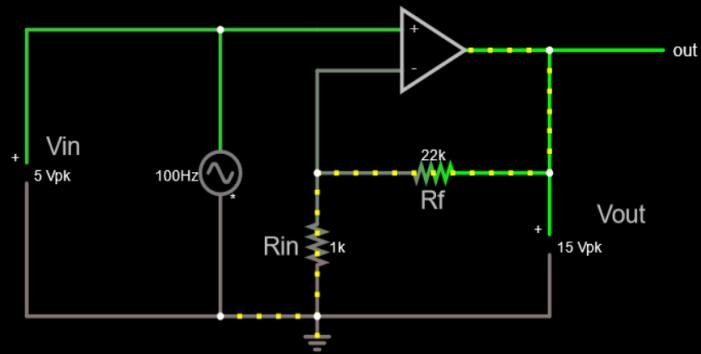

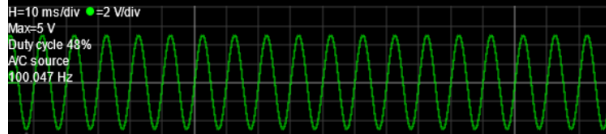H=10 ms/div  $\bullet$ =2 V/div  
Max=5 V  
Duty cycle 48%  
A/C source  
100.047 Hz



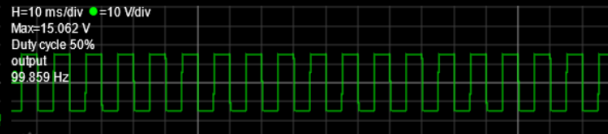
H=10 ms/div  $\bullet$ =10 V/div  
Max=15.062 V  
Duty cycle 50%  
output  
99.859 Hz




output  
V=15 V

12113 Shahmeer


### Non-Inverting-Voltage Amplifier

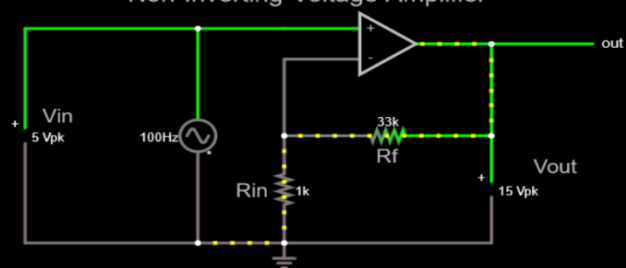

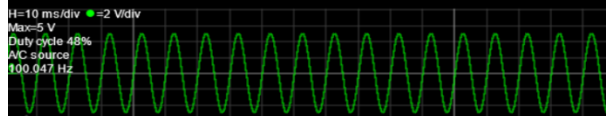H=10 ms/div  $\bullet$ =2 V/div  
Max=5 V  
Duty cycle 48%  
A/C source  
100.047 Hz



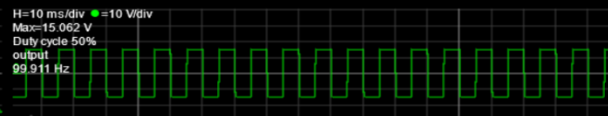
H=10 ms/div  $\bullet$ =10 V/div  
Max=15.062 V  
Duty cycle 50%  
output  
99.911 Hz




output  
V=15 V

12113 Shahmeer


### Non-Inverting-Voltage Amplifier

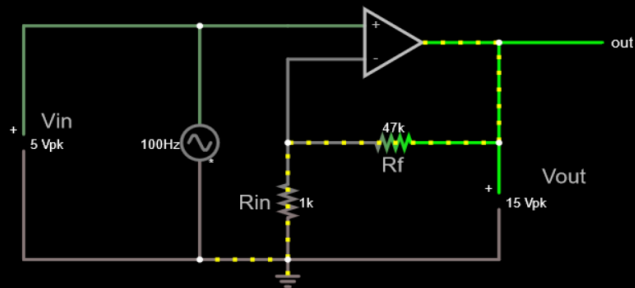

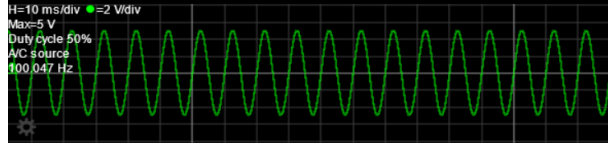H=10 ms/div  $\bullet$ =2 V/div  
Max=5 V  
Duty cycle 50%  
AC source  
100.047 Hz



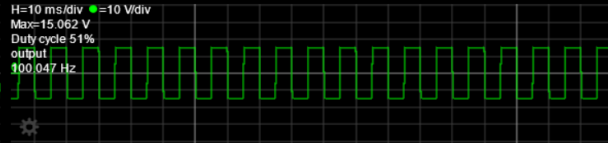H=10 ms/div  $\bullet$ =10 V/div  
Max=15.062 V  
Duty cycle 51%  
output  
100.047 Hz



t=1.33 s  
time step=5  $\mu$ s

**Link:**

<https://tinyurl.com/ydlgqgsk>