

BE LAB TASK # 03

Name: Shahmeer khan.

Student ID: 12113.

Class ID: 106293.

Topic: Series Resistive
Circuit.

Task:

Observations/Calculations:

Objectives:

A, Identify Series Circuit.

B, Calculate and Measure the resistance of a series circuit.

C, Measure the Current Flow in a Series Circuit using an ammeter.

D, Measure the Voltage Drop in a series circuit using Volt Meter.

Objective A:

Identify Series Circuit;

EXERCISE PROCEDURE:

OBJECTIVE A: Identify series circuit

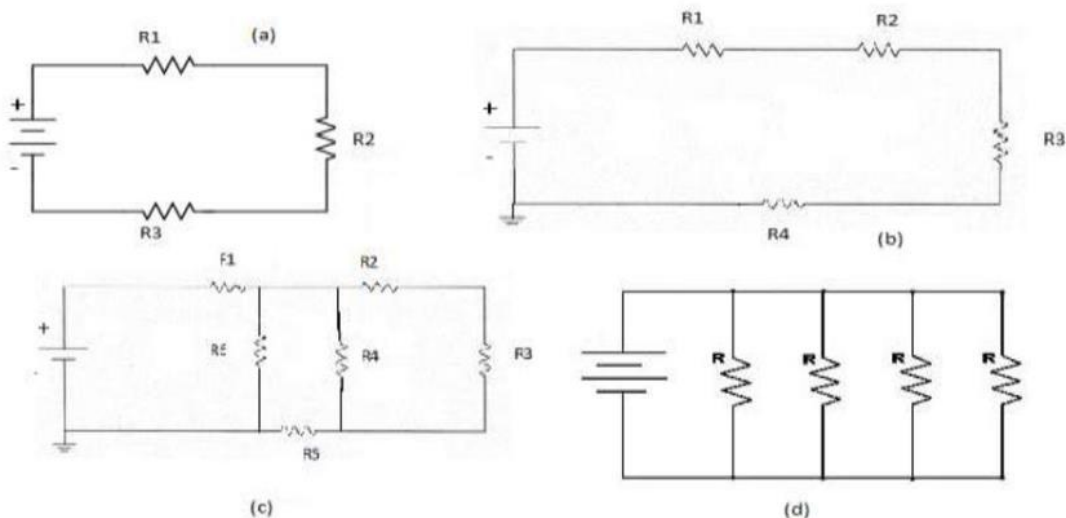


FIG-1

Answer: a and b.

Objective B:

Calculate and Measure the resistance of a series circuit.

RESISTOR	COLOR CODE (COLORS)	INDICATED VALUE (OHMS)	TOLERANCE (PERCENT)	MEASURED VALUE (OHMS)
R1	Brown, Black, Red, Gold.	1000	5	1000
R2	Brown, BLACK, BROWN, Gold.	100	5	100
R3	Brown, GREEN, Red, SILVER.	1500	10	1500

*Record in Table, the color code, indicated value and tolerance and each resistor R1 through R3.

*Use multi-meter to measure of each resistor and enter them in Table.

*Adding the indicated value together, calculate total resistance,

$R_{T \text{ (INDICATED)}}$.

$$R_{T \text{ (INDICATED)}} = 2600 \text{ Ohms.}$$

*Adding the measured value together, calculate total resistance,


$R_{T \text{ (MEASURED)}}$.

$$R_{T \text{ (MEASURED)}} = 2600 \text{ Ohms.}$$

*Is the indicated resistance value $R_{T \text{ (INDICATED)}}$ the same as the total measured value $R_{T \text{ (MEASURED)}}$?

Answer: Yes.

SS of above work:

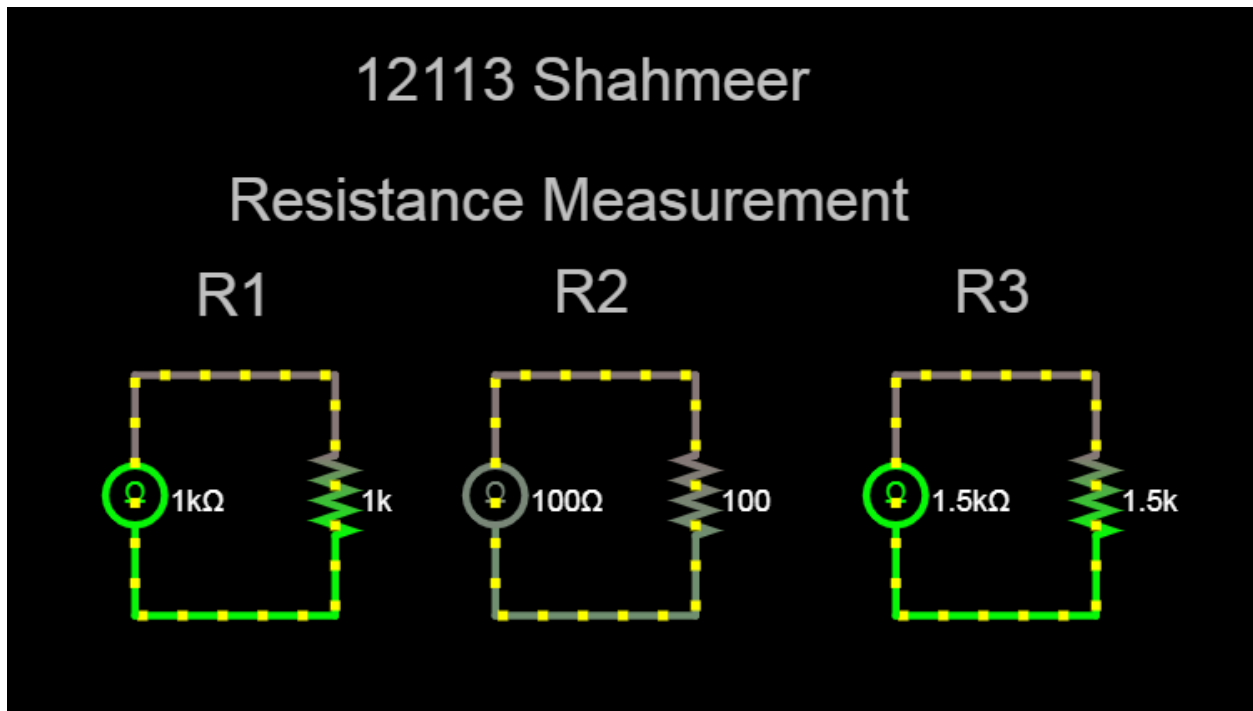


*Connect resistor R1 through R3 in series. Measure the total circuit resistance R_T with ohmmeter.

$$R_{T \text{ (Circuit)}} = 2.6K \text{ Ohms.}$$

Or

$$R_{T \text{ (Circuit)}} = 2600 \text{ Ohms.}$$

SS of above work:

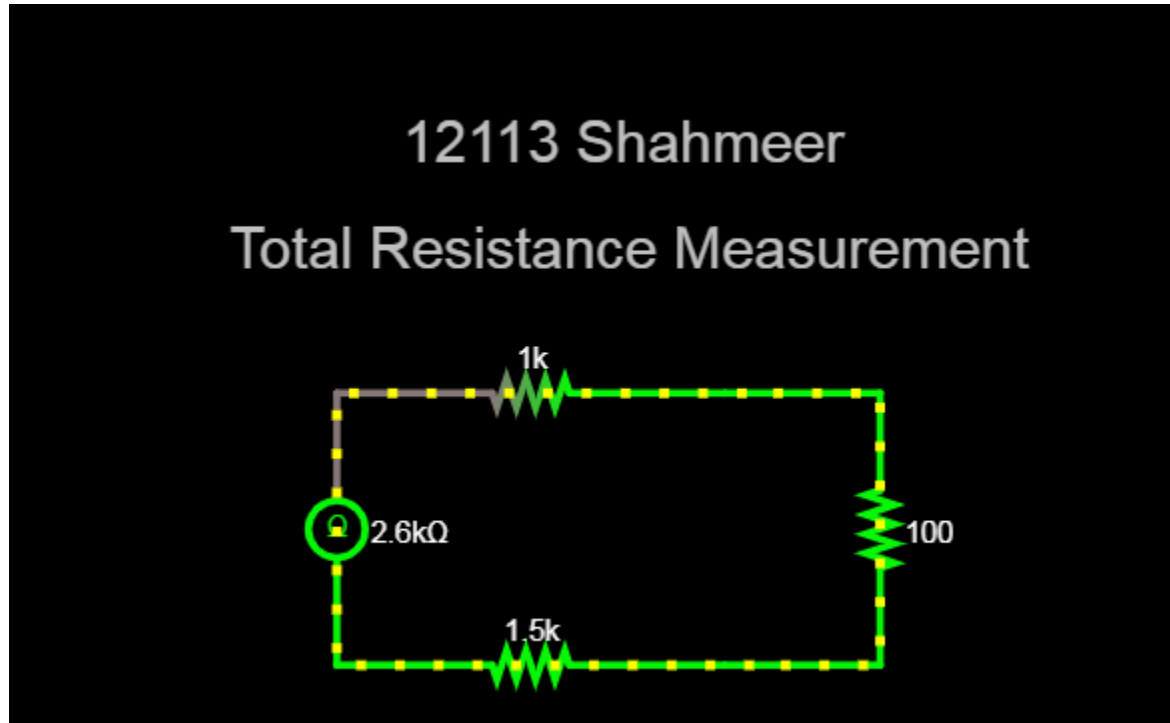


*Does the total resistance value, $R_{T(CIRCUIT)}$ agrees with the result of above exercise?

Answer: Yes.

Objective C:

Measure the Current Flow in a Series Circuit using an ammeter.

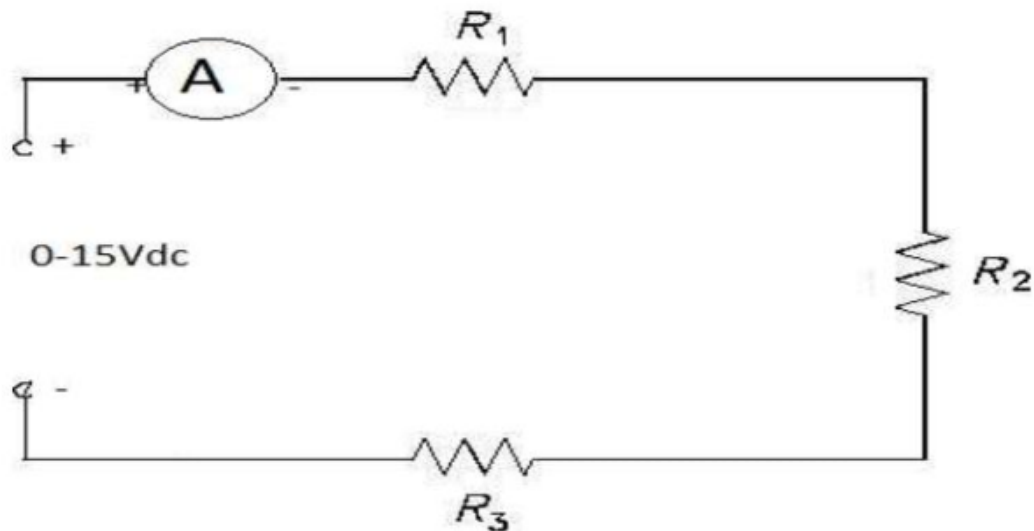
*Connect the circuit shown in Figure. Note that the ammeter, set to the 0-10mA dc range, is connected in series with the resistor R₁ and the power source.



*Adjust the power supply to 10Vdc. How much circuit current is indicated by the milli ammeter?

$$I_{\text{(Circuit)}} = 3.846 \text{ mA DC.}$$

SS of above work:

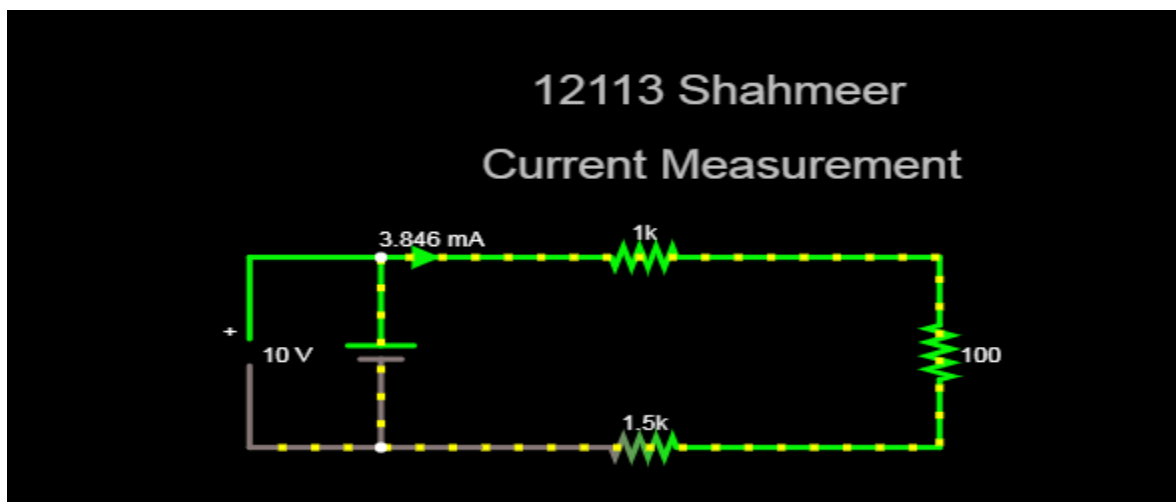

*Return the voltage to zero.

*You can also find total circuit resistance by using ohm's law. Substitute the applied voltage and the circuit current measured above into Ohm's Law formula $R=V/I$ to calculate the total circuit resistance,

R_T (Circuit)

Answer:

$R=??$

$V=10$ vdc.

$I=3.846$ mA dc.

$R=V/I$.

$R=10/ 0.003846$.

$R=2600.104004$ Ohms.

$R=2600$ Ohms. (Final Form after rounding off).

*Does the total calculated circuit resistance value, R_T (CALCULATED) agrees with the result of above calculated value?

Answer: Yes but a little bit not perfect but after rounding off it will be.

*List the possible factors that could account for the results not being in perfect argument.

Answer: *Tolerance.

*Human Error.

*Instrumental error/issue.

*Now measure the current at different locations, throughout the series circuit. Connect the milli-ammeter between R1 and R2.

*Adjust the power source to 10Vdc.

*Measure and record the current flowing between R1 and R2

$$I_{(R1-R2)} = 3.846 \text{ mA DC.}$$


*Repeat last step with the mill ammeter connected, in turn to the following circuit positions:

$$I_{(R1-R2)} = 3.846 \text{ mA DC.}$$

$$I_{(R2-R3)} = 3.846 \text{ mA DC.}$$

$$I_{(R3-PS)} = 3.846 \text{ mA DC.}$$

SS of above work:

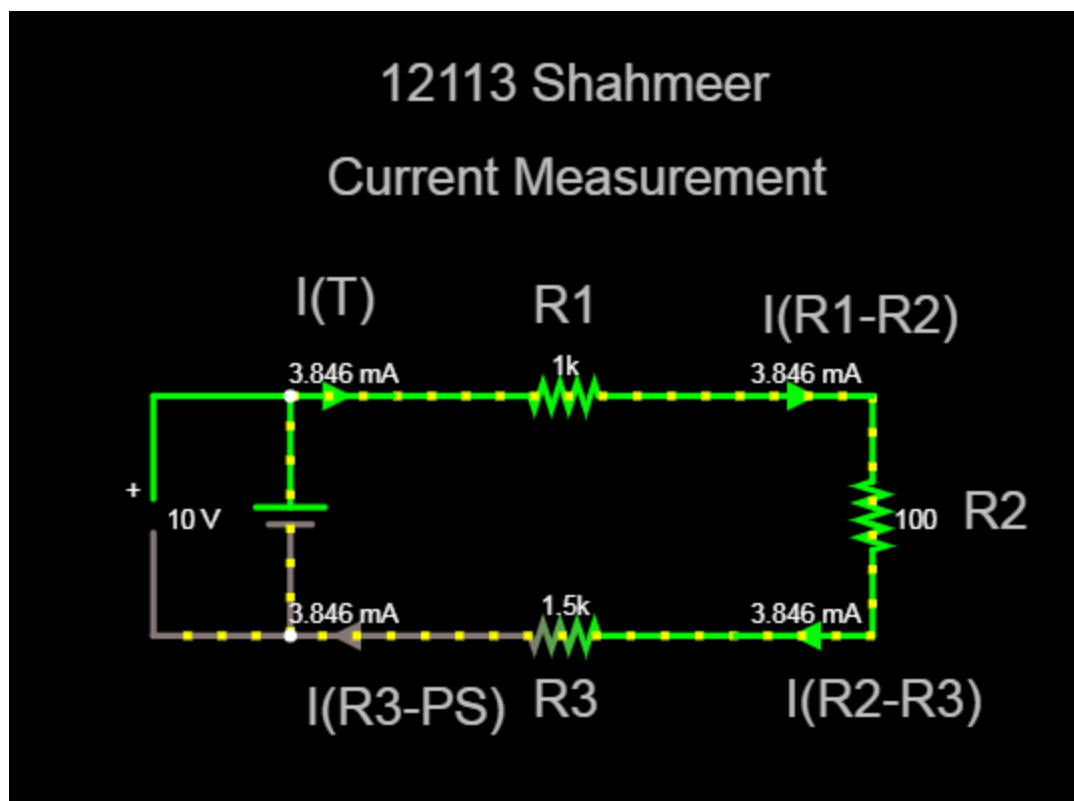

Compare the current values at different locations. Are they the same?

Answer: Yes.

Objective D:

Measure the Voltage Drop in a series circuit using Volt Meter.

$$V_{R1} = 3.846 \text{ VDC.}$$

$$V_{R2} = 0.384615 \text{ VDC.}$$

$$V_{R3} = 5.769 \text{ VDC.}$$

Compare the Voltage values at different locations. Are they the same?

Answer: NO.


*What important rule of the series circuit have you verified?

Answer: *Voltage changes with respect to the resistors in series at different points.

*Current (I) remains the same in series circuit.

*Resistance increases.

SS of above work:

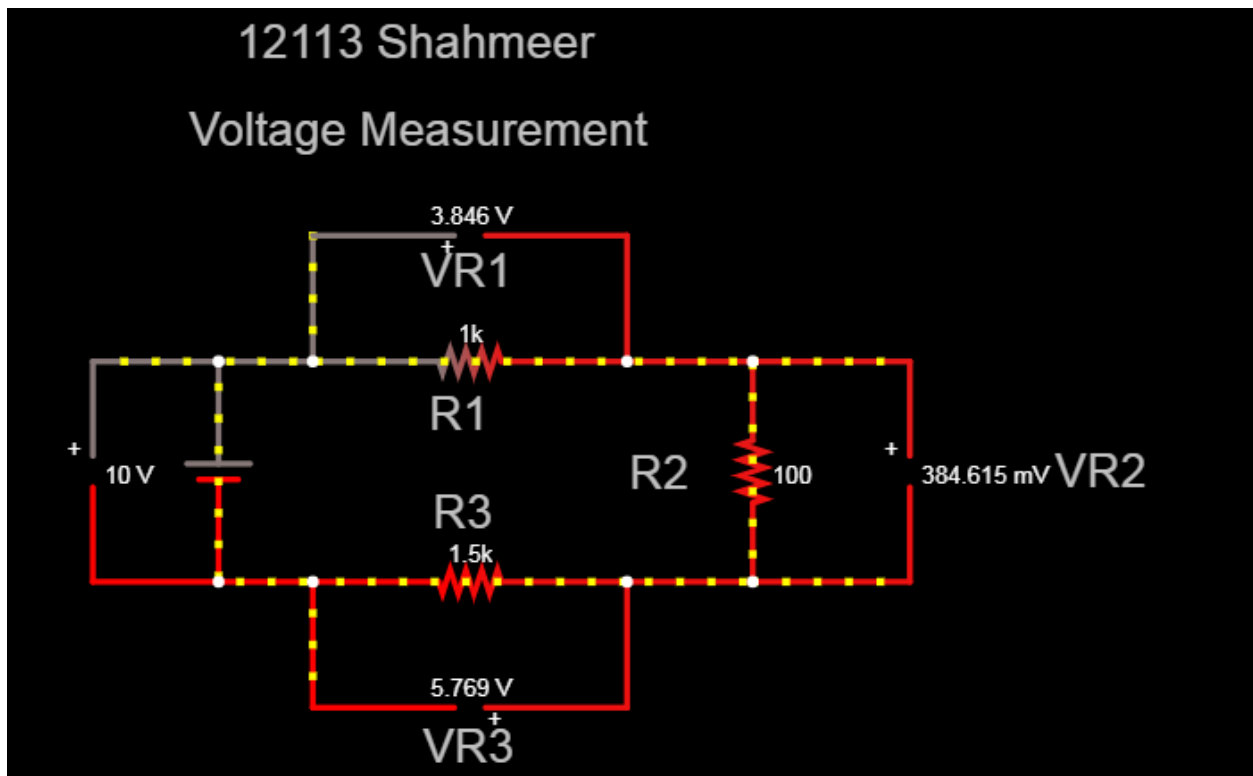

LINK:

<https://tinyurl.com/yxfxdl8b>