

BE LAB TASK # 10

Name: Shahmeer khan.

Class ID: 106293.

Student ID: 12113.


Topic: Full Wave
Rectifier

Objectives:-


- To study the use of four Diodes in a bridge as a Full Wave Rectification.

Lab Task:

- Connect the circuit as shown in fig-2:

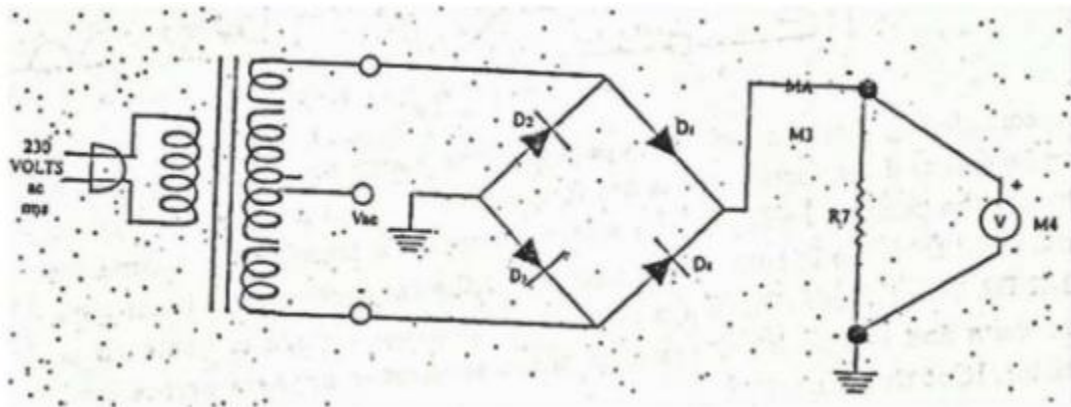

- SCREENSHOT of Circuit as asked:

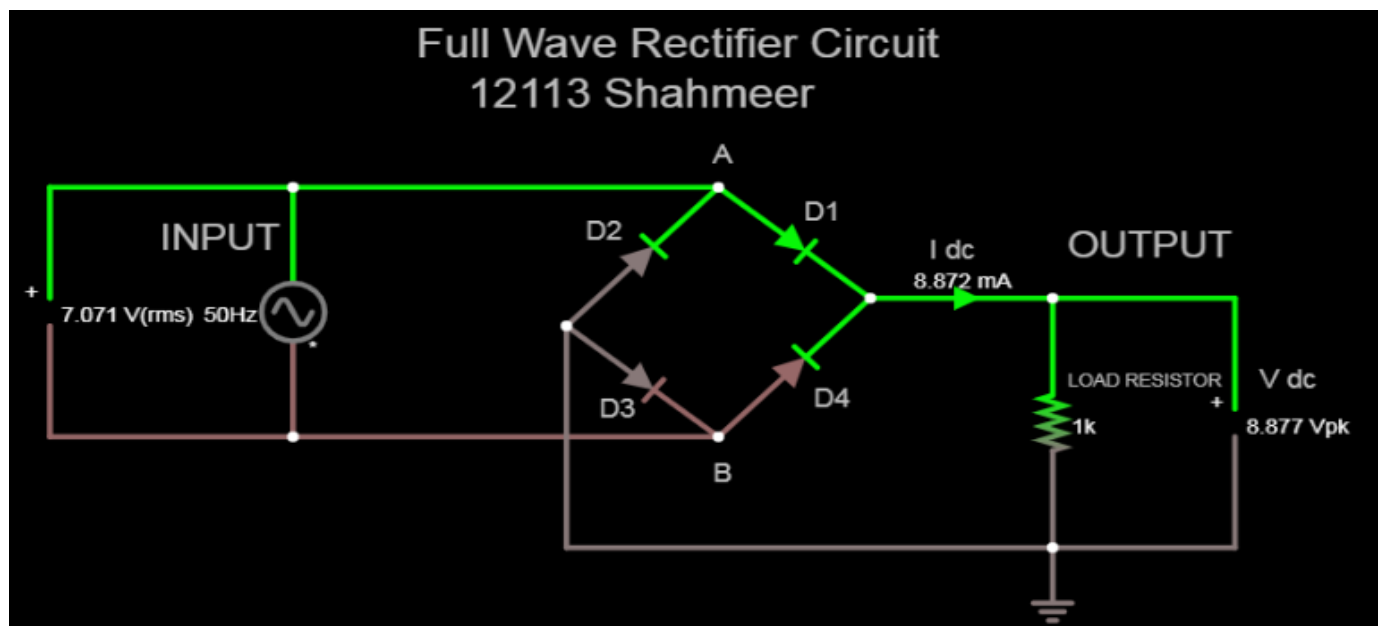

5. Use the function of Voltmeter at 10 volts ac.

6. Use UT55 to measure the Ac Voltage, V_{ac} across the Output terminals of the Voltage transformer. Voltmeter will read the Rms value of the Ac voltage.

$$V_{ac} = 7.071 \text{ volts}$$

7. Measure the dc current, indicated on Ampere meter DC. This will be equal to the average value of full wave rectified current, I_{av} , through the load resistor, R_1 .

$$I_{dc} = 8.872 \text{ m Amp.}$$

8. Measure the dc voltage V_{dc} , across the load resistor, R_1 , indicated by the dc voltmeter, on the trainer.

$$V_{dc} = 8.877 \text{ volts.}$$

9. Calculate the peak value, V_p of the Ac input voltages measured in Step 6.

Since Formula:

$$V_p = V_{ac} / 0.707$$

$$7.071 / 0.707$$

$$V_p = 10.00 \text{ volts.}$$

10. Calculate the peak current I_p , through the load resistor R_1 , from the current measured in Step 7.

Since Formula:

$$I_p = V_{dc} / R$$

$$8.877 / 1000$$

$$I_p = 8.877 \text{ m Amp.}$$

11. Calculate the average value of the full wave rectified output voltage across the load resistor R_1 , also check that this value corresponds with the value of V_{dc} obtained in step 8, this is given by $V_{av} = I_{dc} * R_1$.

Since Formula:

$$V_{av} = I_{dc} * R$$

$$(8.872 \times 10^{-3}) \times 1000$$

$$V_{av}(\text{out}) = 8.877 \text{ volts.}$$

12. Calculate the V_d value (half cycle average) of the input voltage from the maximum value V_p by using.

$$V_{dc} = 0.636 * V_p$$

$$V_{dc} = 0.636 * 10$$

$$V_{dc}(\text{in}) = 6.36 \text{ volts.}$$

13. Refer to step 8 for the average value of the Output dc voltage developed across R_1 , Subtract this value from the dc value of the input voltage V_{dc} obtained in step 12.

(Step 12 – Step 8)

$$6.36 - 8.77$$

$$V(\text{diff}) = -2.41 \text{ volts.}$$

14. Refer to the V-I characteristics obtained in diode experiment. Determine the voltage drop across the diode which corresponds to the dc current through the diode, obtained in Step 7.

(Step 9 – Step 8)


$$10.00 - 8.87$$

$$V_{\text{diode}} = 1.123 \text{ volts}$$

15. While the coupling switch is in DC Position. Draw the waveforms displayed on the oscilloscope in Scope Chart shown below.

Indicate the peak, rms, and the average of the full-wave rectified output voltage waveform as well as the input voltage waveform.

- SCREENSHOT of input waveform:

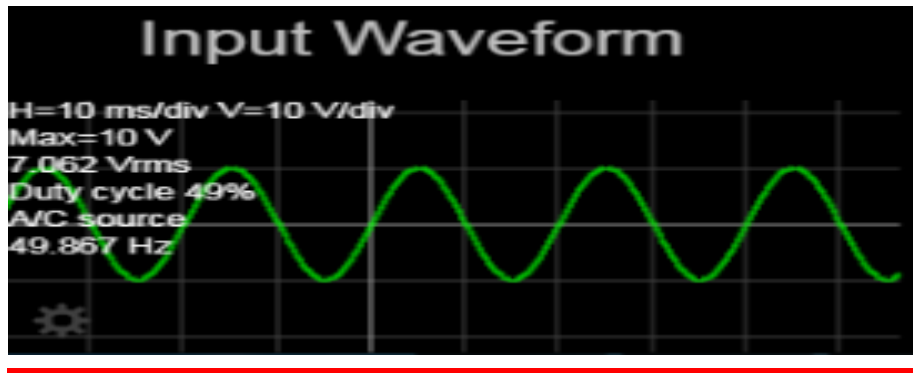

Voltage Sensitivity = 10 volts/div

Time Per Division = 10 msec/div

* INPUT VOLTAGE WAVEFORM

Since: $V_p = 10$ volts

Peak to Peak Voltages

$$V_{p-p} = V_p \times 2$$

$$V_{p-p} = 10 \times 2 = 20 \text{ volts}$$

$$V_{rms} = 0.707 \times V_p$$

$$0.707 \times 10$$


$$V_{rms} = 7.07 \text{ volts}$$

$$V_{av} = V_p(\text{output}) \times 0.636$$

$$10 \times 0.636$$

$$V_{av} = 6.36 \text{ volts}$$

- SCREENSHOT of Output WaveForm:

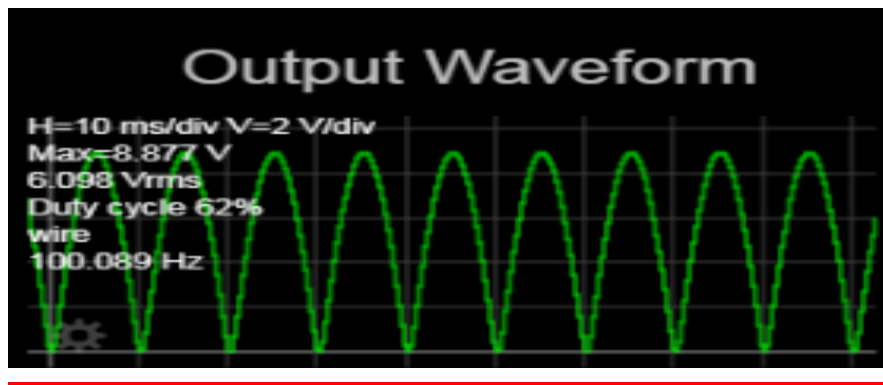


- OUTPUT VOLTAGE WAVEFORM

$V_p = 8.877$ volts


$V_{av} = 5.645$ volts

$V_{rms} = 8.877$ volts

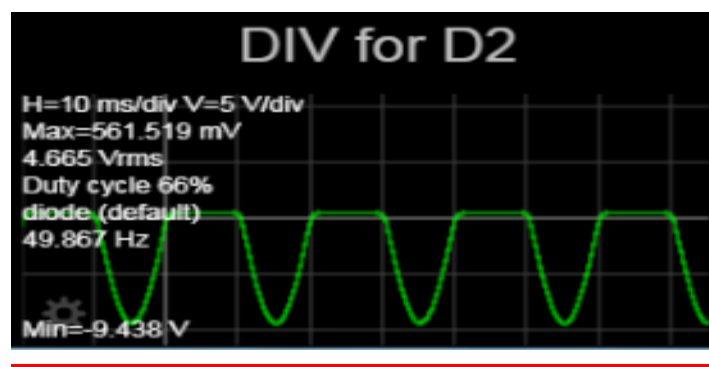16. Connect the probes of the oscilloscope at the nodes between D1 & D2 and b/w D3 and D4. Connect the ground lead of one probes the nodes b/w D3 and D2. Draw the wave from and measure peak values. These are the PIV values across the diodes.




PIV (D2) = 561.519 m volts

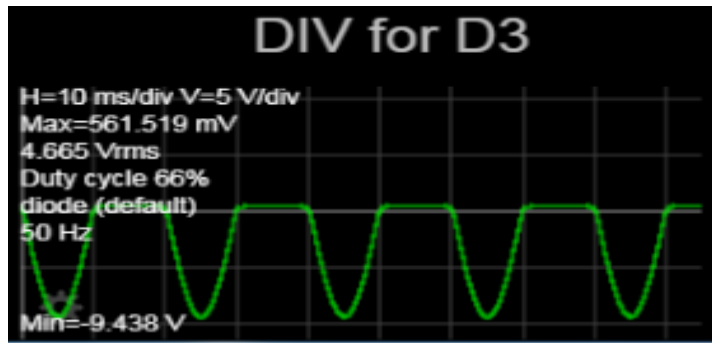

PIV (D3) = 561.519 m volts

- Screenshot of whole circuit:

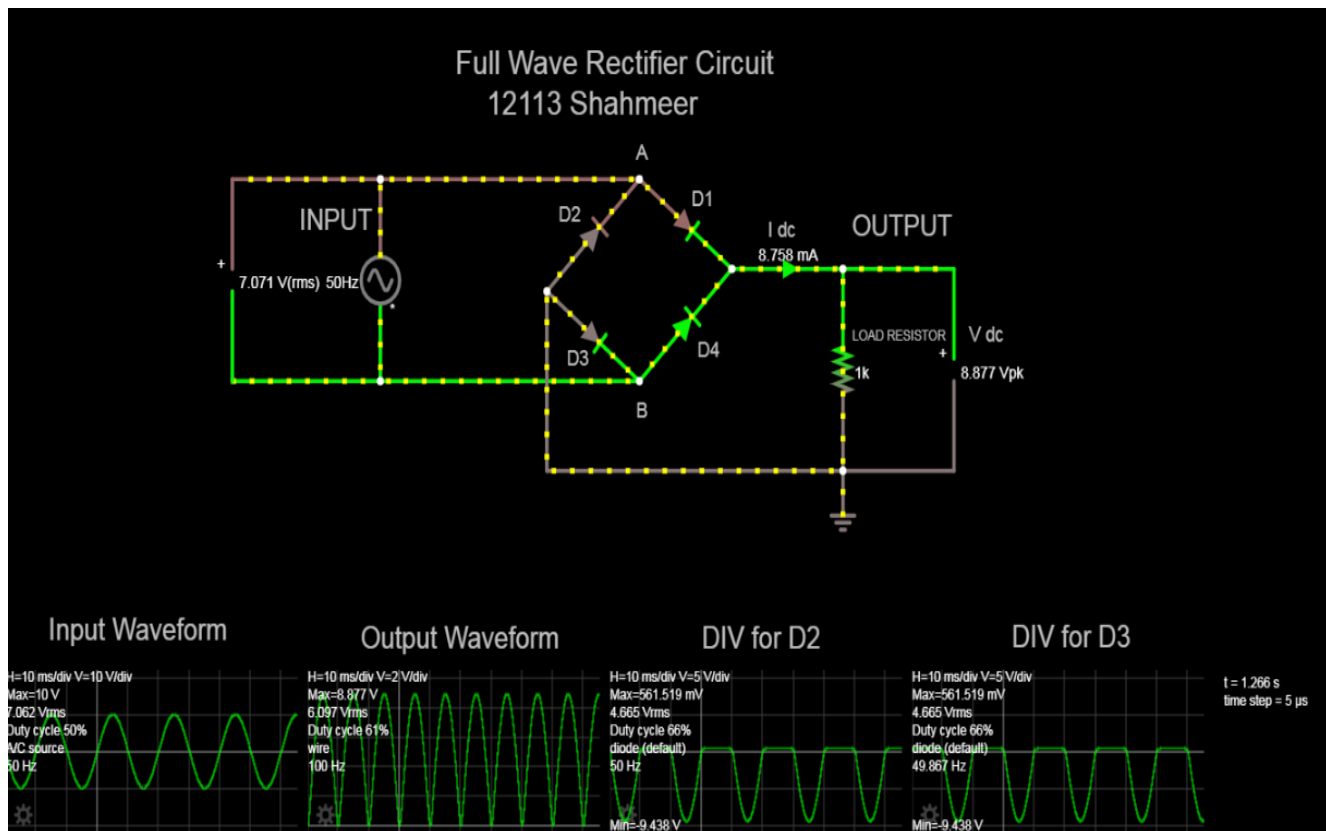

- **Link of Simulator:**

<https://tinyurl.com/yhqpsbub>