

# **BE Theory Assignment # 01**

**Name: Shahmeer khan.**

**Student Id: 12113.**

**Class ID: 106228.**

**(ON NEXT PAGE)**

# BE Assignment #01

Name: Shahmeer Khan


Student ID: 121153

Class ID: 106228

Questions from Grob's Basic Electronics Pg #191  
(11<sup>th</sup> Edition).


Problem 6-9:

Q: In Fig. 6-20:

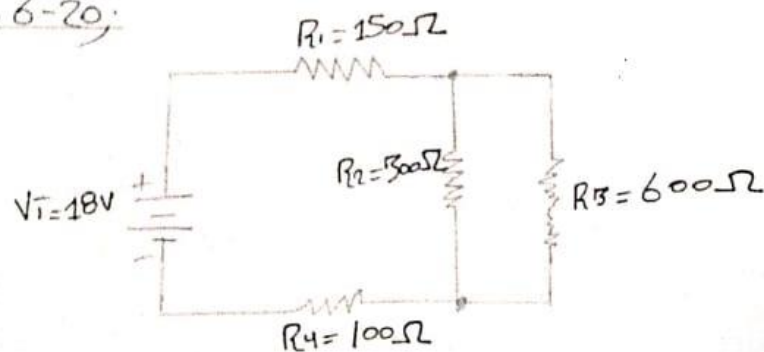

(Fig. 6-20)

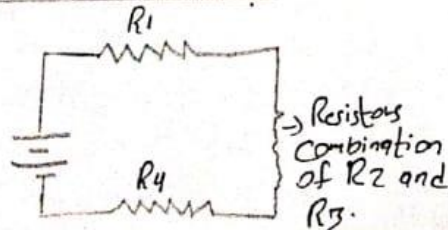a) Total Resistance of  $R_1$  and  $R_4$ ?



Solution:

$\therefore R_1$  and  $R_4$  are connected in Series.


$\therefore R_{1+4} = R_1 + R_4$

$\Rightarrow$  On next page.

$$\Rightarrow R_{1+4} = 150\Omega + 100\Omega$$

$$\Rightarrow R_{1+4} = 250\Omega \underline{\text{Ans.}}$$

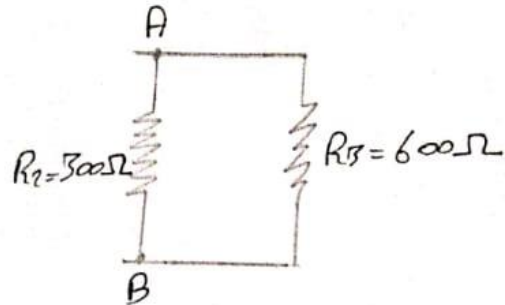b) Equivalent Resistance of  $R_2$  and  $R_3$  across points AB?



Solution;

$\therefore R_2$  and  $R_3$  are connected in Parallel.

$\therefore$  Formula will be used here is;

$$\frac{1}{R_1} = \frac{1}{R_1} + \frac{1}{R_2} + \dots + \frac{1}{R_n}$$

$$\therefore \frac{1}{R_{T_2}} = \frac{1}{R_2} + \frac{1}{R_3}$$

$$\frac{1}{R_{T_2}} = \frac{1}{300} + \frac{1}{600}$$

$$\frac{1}{R_{T_2}} = \frac{600 + 300}{(300)(600)}$$

$$\frac{1}{R_{T_2}} = \frac{900}{180000}$$


$$\frac{1}{R_{T_2}} = \frac{9}{1800}$$

$$\frac{1}{R_{T_2}} = \frac{1}{200}$$

$$\boxed{R_{T_2} = 200\Omega} \underline{\text{Ans.}}$$

c) Total Resistance,  $R_T$ ?

(On next page).

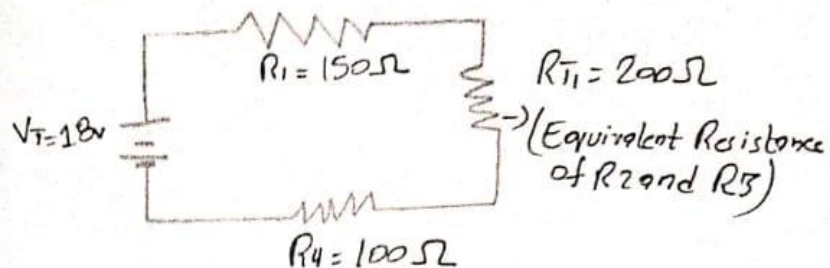

Solution;

$\therefore R_1, R_T$  and  $R_4$  are in Series now So;

$\therefore$  Formula;

$$\therefore R_T = R_1 + R_T + R_4$$

$$\Rightarrow R_T = 150 + 200 + 100$$

$$\Rightarrow \boxed{R_T = 450\Omega} \underline{\underline{Ans.}}$$

d) Total current in the circuit,  $I_T$ ?

Solution;

To calculate Current ( $I_T$ ), using Ohm's law;

$$\therefore V = IR \text{ (Ohm's law)}$$

$$\therefore V_T = I_T R_T$$

$$\Rightarrow 18 = I_T (450) \quad \therefore \boxed{V_T = 18V}, \boxed{R_T = 450\Omega}$$

$$\Rightarrow I_T = \frac{18}{450}$$

$$\Rightarrow \boxed{I_T = 0.04 \text{ amp.}} \underline{\underline{Ans.}}$$

e) How much current flows into point B and away from point A?

Ans; If we are finding Current's Intensity through a specific path on the circuit, first we need voltage of that component. For that we use "Voltage divider formula".

$$\Rightarrow \text{Voltage divider formula} = V_i = \frac{R_i}{R_1 + R_2 + R_3} (V_{\text{Total}})$$

(Rem. part on next page).



∴ Now, calculating voltage across point A and B;

∴ Substituting the components;

$$V_{AB} = \left( \frac{R_{T1}}{R_1 + R_4 + R_{T1}} \right) (V_{Total})$$

∴ Here,  $R_{T1}$  is the combined resistance of 2 parallel circuits  $R_2$  and  $R_1$ , which is  $200\Omega$ .

$$\therefore V_{AB} = \left( \frac{200}{150 + 200 + 200} \right) (18)$$

$$\Rightarrow \boxed{V_{AB} = 8 \text{ volts}} \underline{\underline{Ans.}}$$

∴ Now we know voltage that flows across A and B ( $V_{AB}$ ),  $V_{AB} = 8 \text{ volts}$ , and the resistance through  $R_2$ ,  $R_2 = 500\Omega$

∴ Now finding current ( $I_{AB}$ ) across A and B;

$$\therefore V_{AB} = I_{AB} \cdot R_2$$

$$I_{AB} = \frac{V_{AB}}{R_2}$$

$$I_{AB} = \frac{8}{500}$$

$$\boxed{I_{AB} = 0.0266 \text{ amp.}} \underline{\underline{Ans.}}$$

### Problem 6-12;

Q. In Fig. 6-22;

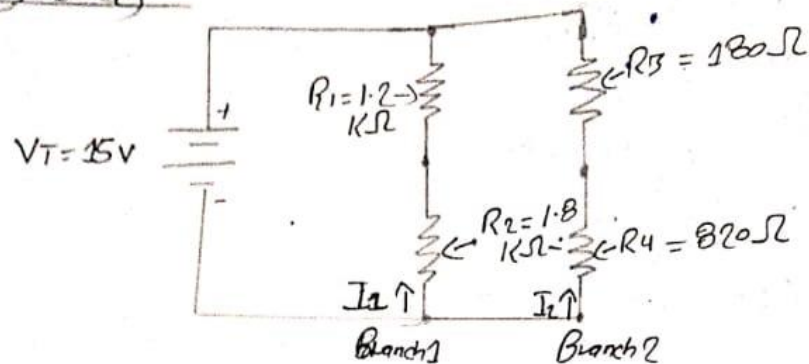


Fig. 6-22.

a) Total Resistance of branch 1?

Solution;

∴ Considering that the both resistors are connected in series.

$$\therefore R_{B1} = R_1 + R_2$$

$$\Rightarrow R_{B1} = 1.2K\Omega + 1.8K\Omega$$

$$\Rightarrow \boxed{R_{B1} = 3000\Omega} \underline{\underline{Ans}}$$

b) Total Resistance across Branch 2?

Solution;

∴ Also here considering both resistors are connected in series.

$$\therefore R_{B2} = R_3 + R_4$$

$$\Rightarrow R_{B2} = 180 + 820$$

$$\Rightarrow \boxed{R_{B2} = 1000\Omega} \underline{\underline{Ans}}$$

c) Branch Currents  $I_1$  and  $I_2$ ?

Solution;

∴ Current is parallel, so Voltage will be same everywhere.

(On next page)

① For  $I_1$ ,

∴ Using Ohm's Law;

$$V_T = I_1 R_{B1}$$

$$15 = I_1 (R_1 + R_2)$$

$$15 = I_1 (1200 + 1800)$$

$$15 = I_1 (3000)$$

$$\boxed{I_1 = 0.005 \text{ amp.}} \quad \underline{Ans.}$$

② For  $I_2$ ,

∴ Using Ohm's Law;

$$V_T = I_2 R_{B2}$$

$$15 = I_2 (1000)$$

$$I_2 = \frac{15}{1000}$$

$$\boxed{I_2 = 0.015 \text{ amp.}} \quad \underline{Ans.}$$

d) Total current of the circuit?  $I_T$ ?

Solution;

$$\therefore \text{Total current} = I_T = I_1 + I_2$$

$$\Rightarrow I_T = 0.005 \text{ amp} + 0.015 \text{ amp}$$

$$\Rightarrow I_T = 5 \text{ m.amp} + 15 \text{ m.amp}$$

$$\Rightarrow \boxed{I_T = 20 \text{ m.amp. or } 0.02 \text{ amp.}} \quad \underline{Ans.}$$

e) Total Resistance ( $R_T$ ) of the circuit?

Solution;

$$\therefore \text{Total Resistance of circuit} = R_T = \frac{1}{R_{B1}} + \frac{1}{R_{B2}} \quad (\because \text{Since the branches are in parallel})$$

(Connect page):



$$\Rightarrow \frac{1}{R_T} = \frac{1}{R_{B1}} + \frac{1}{R_{B2}}$$

$$\Rightarrow \frac{1}{R_T} = \frac{1}{3000} + \frac{1}{1000}$$

$$\Rightarrow \frac{1}{R_T} = \frac{1}{750}$$

$$\Rightarrow \boxed{R_T = 750 \Omega} \underline{\underline{Ans.}}$$

f) Values of  $V_1$ ,  $V_2$ ,  $V_3$  and  $V_4$ ?

Solution;

①  $\therefore$  For that, for each we will be using voltage divider formula.

① For  $V_1$ ;

$$V_1 = \frac{R_1}{R_1 + R_2} (V_T)$$

$$V_1 = \frac{1200}{1200 + 1800} (15)$$

$$\boxed{V_1 = 6V} \underline{\underline{Ans.}}$$

① For  $V_2$ ;

$$V_2 = \frac{R_2}{R_1 + R_2} (V_T)$$

$$V_2 = \frac{1800}{1200 + 1800} (15)$$

$$\boxed{V_2 = 9V} \underline{\underline{Ans.}}$$

① for  $V_3$ ;

$$V_3 = \frac{R_3}{R_3 + R_4} (V_T)$$

$$V_3 = \frac{180}{180 + 820} (15)$$

$$\boxed{V_3 = 2.7V} \underline{\underline{Ans.}}$$

① For  $V_4$ ;

$$V_4 = \frac{R_4}{R_3 + R_4} (V_T)$$

$$V_4 = \frac{820}{180 + 820} (15)$$

$$\boxed{V_4 = 12.5V} \underline{\underline{Ans.}}$$



Problem 6-20;

Q; In Fig. 6-30;

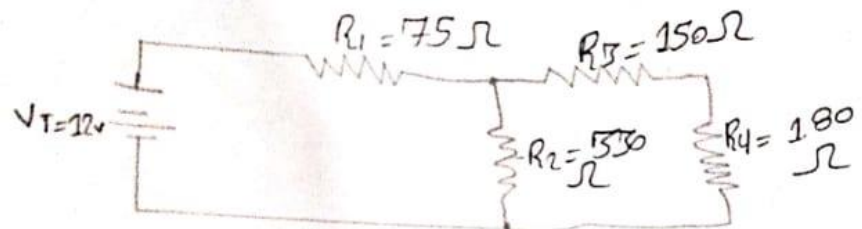


Fig. 6-30;

Q; In Fig. 6-30, Solve for  $R_T$ ,  $I_T$ ,  $V_1$ ,  $V_2$ ,  $V_3$ ,  $V_4$ ,  $I_1$ ,  $I_2$ ,  $I_3$  and  $I_4$ .

Solution;

○ For  $R_T$ ;

i)  $R_{34}$ ; ( $\therefore$  Since it is in series).

$$R_{34} = R_3 + R_4$$

$$R_{34} = 150 + 180$$

$$\boxed{R_{34} = 330\Omega}$$

ii)  $R_{234}$ ; ( $\therefore$  Since  $R_2$  and  $R_{34}$  are in parallel).

$$\frac{1}{R_{234}} = \frac{1}{R_2} + \frac{1}{R_{34}}$$

$$= \frac{1}{530} + \frac{1}{330}$$

$$\frac{1}{R_{234}} = \frac{1}{165}$$

$$\boxed{R_{234} = 165\Omega}$$

○  $R_T = R_{1234}$  ( $\therefore$  Since  $R_1$  and  $R_{234}$  are in series).

$$R_T = R_1 + R_{234}$$

$$\boxed{R_T = 75 + 165 = 240\Omega} \underline{Ans.}$$

① For  $I_T$ :

∴ Using Ohm's law,

$$\therefore V_T = I_T R_T$$

$$I_T = \frac{V_T}{R_T}$$

$$I_T = \frac{12}{240} \quad \therefore (R_T = 240 \Omega) \quad (V_T = 12V)$$

$$I_T = 0.050A \quad \underline{\underline{Ans.}}$$

OR;

$$I_T = 50mA \quad \underline{\underline{Ans.}}$$

② For  $V_1$ :

∴ Using voltage divider formula;

$$V_1 = \frac{R_1}{R_1 + R_{234}} (V_T)$$

$$V_1 = \frac{75}{75 + 165} (12)$$

$$V_1 = 3.75V \quad \underline{\underline{Ans.}}$$

③ For  $V_2$ :

∴ For that again using voltage divider formula.

$$V_2 = \frac{R_{234}}{R_1 + R_{234}} (V_T)$$


$$V_2 = \frac{165}{75 + 165} (12)$$

$$V_2 = 8.25V \quad \underline{\underline{Ans.}}$$

(On next page)

① For  $V_3$ ;

∴ To calculate  $V_3$

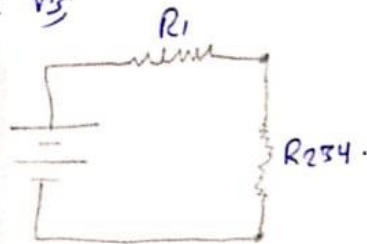

∴ For  $V_3$  first we have to calculate the current using Kirchhoff law.

$$\therefore I_T = I_1 + I_2 + I_3$$

∴ Current divider formula;

$$\therefore I_1 = \frac{R_T}{R_1} (I_T)$$

$$I_1 = \frac{240}{75} (0.05)$$

$$\textcircled{I_1 = 0.16 \text{ A}}$$

① For  $I_2$ ;

$$I_2 = \frac{R_T}{R_2} (I_T)$$

$$I_2 = \frac{240}{530} (0.05)$$

$$\textcircled{I_2 = 0.036 \text{ A}}$$

① For  $I_3$ ;

$$I_3 = \frac{R_T}{R_3} (I_T)$$

$$\textcircled{I_3 = 0.08 \text{ A}}$$

① For  $I_4$ ;

$$I_4 = \frac{R_T}{R_4} (I_T)$$

$$\textcircled{I_4 = 0.0667 \text{ A}}$$

① ∴ Now Using these value to find  $V_3$  and  $V_4$ .

① For  $V_3$  (continued);

$$V_3 = I_3 R_3$$

$$V_3 = 0.08 \times 150$$

$$\textcircled{V_3 = 12 \text{ V}}$$

① For  $V_4$ ;

$$V_4 = I_4 \times R_4$$

$$V_4 = 0.0667 \times 180$$

$$\textcircled{V_4 = 12 \text{ V}}$$



# Problem 6-35.

Q. In fig. 6-44, assume that the bridge is balanced when  $R_1 = 1\text{K}\Omega$ ,  $R_3 = 34,080\Omega$ ,  $R_2 = 5\text{K}\Omega$ .

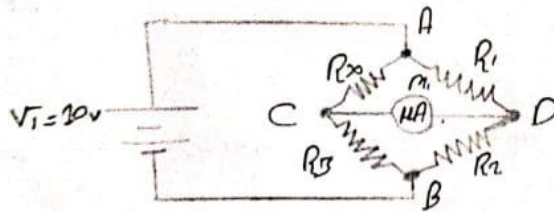


Fig-6-44.

a) The value of the unknown resistor,  $R_x$ , if the bridge is balanced, that means that the Galvanometer reads  $0\mu\text{A}$  at the moment.


Solution;

$\therefore$  Using the Wheatstone bridge formula;

$$\frac{I_1 R_x}{I_2 R_3} = \frac{I_2 R_2}{I_2 R_1} \Rightarrow$$

$$R_x = \frac{R_2}{R_1} (R_3)$$
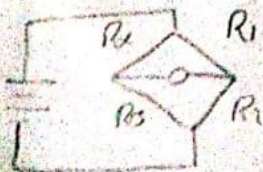
$$\begin{aligned} \therefore R_1 &= 1000\Omega \\ \therefore R_2 &= 5000\Omega \\ \therefore R_3 &= 34,080\Omega \\ \therefore R_x &= ? \end{aligned}$$



$$\frac{I_1 R_x}{I_2 R_3} = \frac{I_2 R_2}{I_2 R_1} \Rightarrow \frac{R_2}{R_1} = \frac{R_3}{R_x}$$


$$\Rightarrow R_x = \frac{R_3}{R_2} \times R_1$$

$$R_x = \frac{1000}{5000} \times 34080$$

$$R_x = 6816\Omega$$




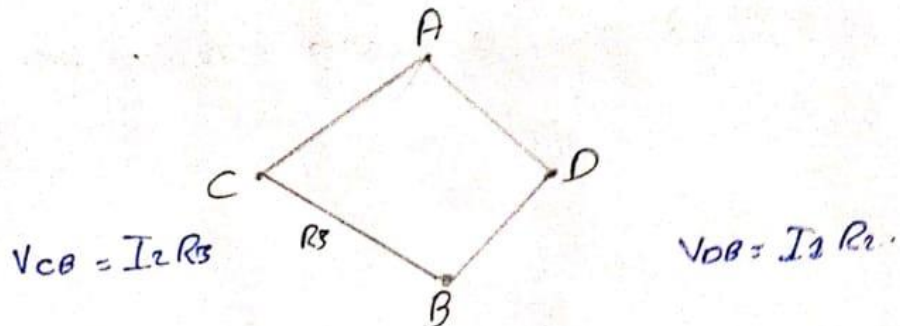b) The voltages  $V_{CB}$  and  $V_{DB}$ .



Solution;

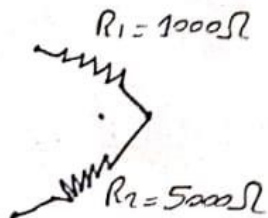To find voltage through components, first we will find  $I_1$  and  $I_2$ .



$\therefore R_1$  and  $R_2$  are in series;

$$V_T = I_1 R_1 R_2 (R_1 + R_2)$$

$$I_1 = \frac{V_T}{R_1 + R_2}$$

$$I_1 = \frac{10}{1000 + 5000}$$

$$I_1 = 1.667 \text{ mA} \quad \text{or} \quad I_1 = 0.001667 \text{ A}$$


Hence  $V_{DB} = V_{at} R_2$ .

$$V_{DB} = I_1 R_2$$

$$V_{DB} = (0.001667)(5000)$$

$$V_{DB} = 8.33 \text{ V}$$

For  $I_2$ ;

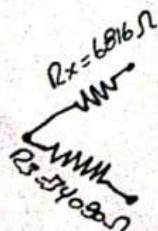

$\therefore R_x$  and  $R_5$  are in series;

$$V_T = I_{R_x R_5} (R_x + R_5)$$

$$I_{R_x R_5} = \frac{V_T}{R_x + R_5}$$

$$I_{R_x R_5} = \frac{10}{6816 + 54080}$$

$$I_{R_x R_5} = 0.000245 \text{ A}$$


Hence  $V_{CB} = V_{at R_5}$

$$V_{CB} = I_{R_5} R_5$$

$$V_{CB} = (0.000245)(54080)$$

$$V_{CB} = 8.53 \text{ V}$$

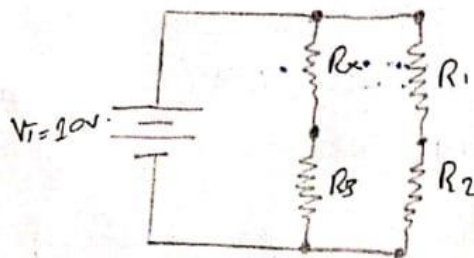c) Total current,  $I_T$ , flowing to and from voltage source:



Answer:

Rearranged the circuit in such a way, that we removed the middle wire, the wire on which Galvanometer was connected, that was done because as we saw, 0V was it P-D and the loadings on Galvanometer showed 0mA. Which means no current passing through that wire. So, while measuring total current, that wire was useless.

i) Calculating the resistance of the circuit.

$\therefore R_1$  and  $R_2$  are in series;

$$R_{12} = R_1 + R_2 = 1000 + 5000$$


$$R_{12} = 6000 \Omega$$

$\therefore R_x$  and  $R_5$  are also in series;

$$R_{5x} = R_x + R_5 = 6816 + 54080$$

$$R_{5x} = 40896 \Omega$$

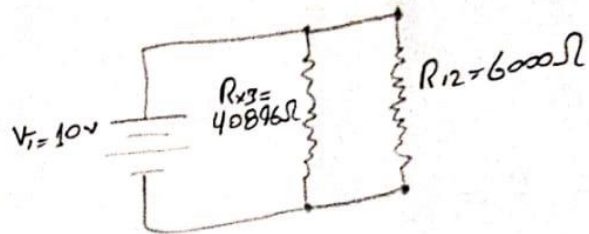Summed up diagram for  $R_{12}$  and  $R_{x3}$ ;



① Now Total Resistance =  $R_T$ ;

$$\frac{1}{R_T} = \frac{1}{R_{12}} + \frac{1}{R_{x3}}$$

∴ (Since  $R_{12}$  and  $R_{x3}$  are now in Parallel)

$$\frac{1}{R_T} = \frac{1}{6000} + \frac{1}{40896}$$

$$\frac{1}{R_T} = \frac{46896}{245376000}$$

$$R_T = 5252.34591 \Omega$$

(ii) Calculating total current ( $I_T$ );

$$V_T = I_T R_T \quad (\because \text{Ohm's Law})$$

$$10 = I_T \times (5252.34591)$$

$$I_T = 1.911 \text{ mA}$$

OR;

$$I_T = 0.0019 \text{ A}$$



**Game SS:**

**(On Next Page)**




1:37 AM

50%
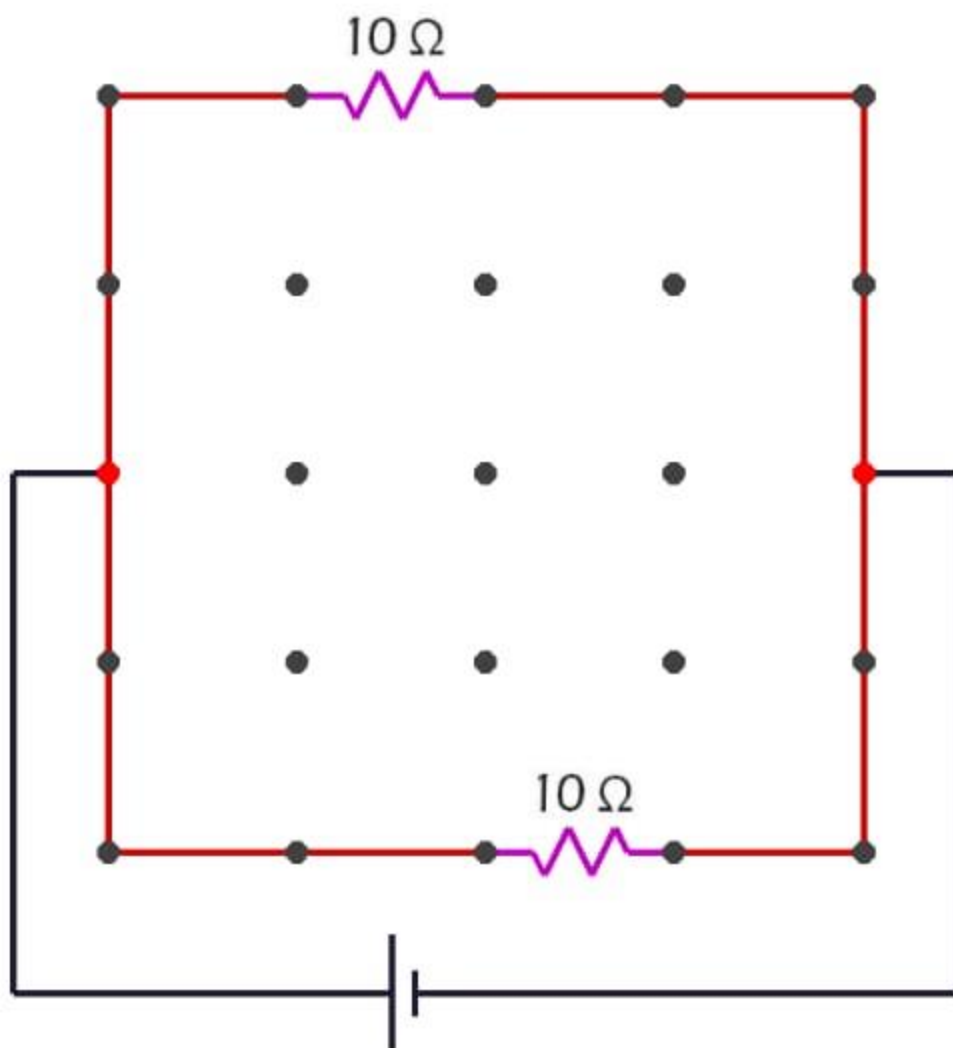
## Level Two

Connect two resistances of 10 ohms each to get an equivalent resistance of 5 ohms.




1:37 AM

5G

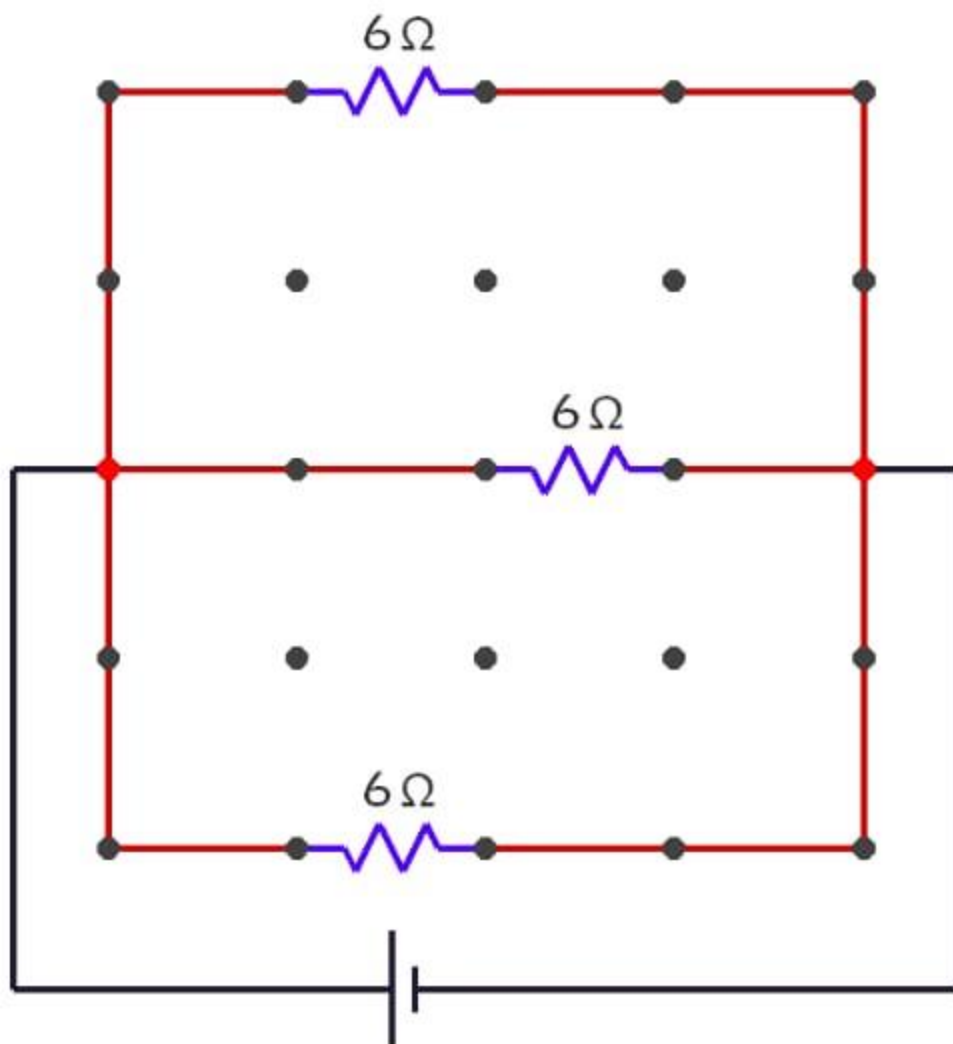
## Level Three

Connect three resistances (6 ohms each) to get an equivalent resistance of 2 ohms.


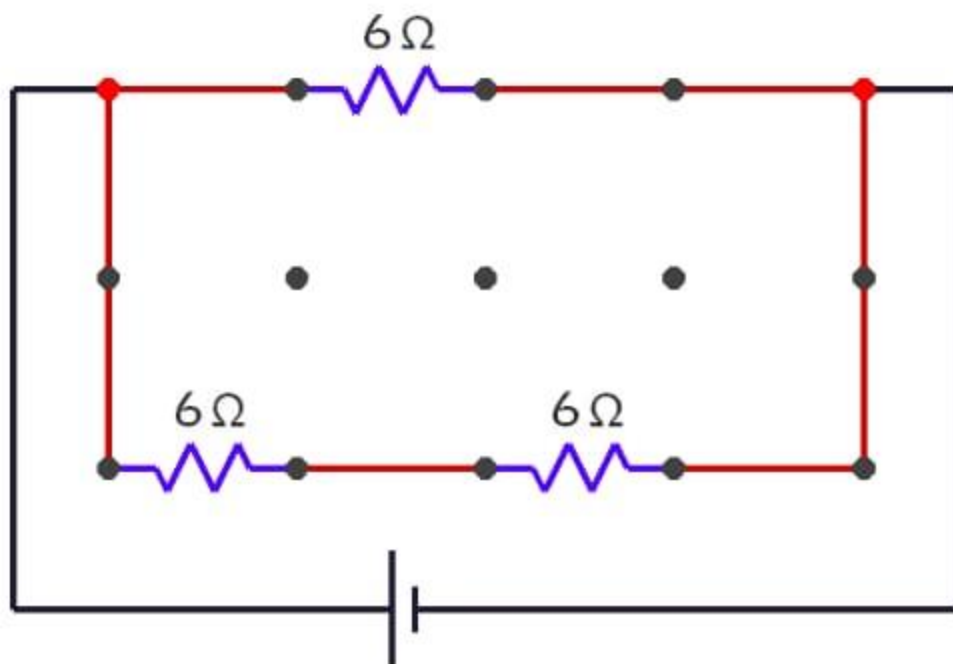
## Level Four

Connect 3 resistances (6 ohms each) to get an equivalent resistance of 4 ohms.




10:21 PM

30%

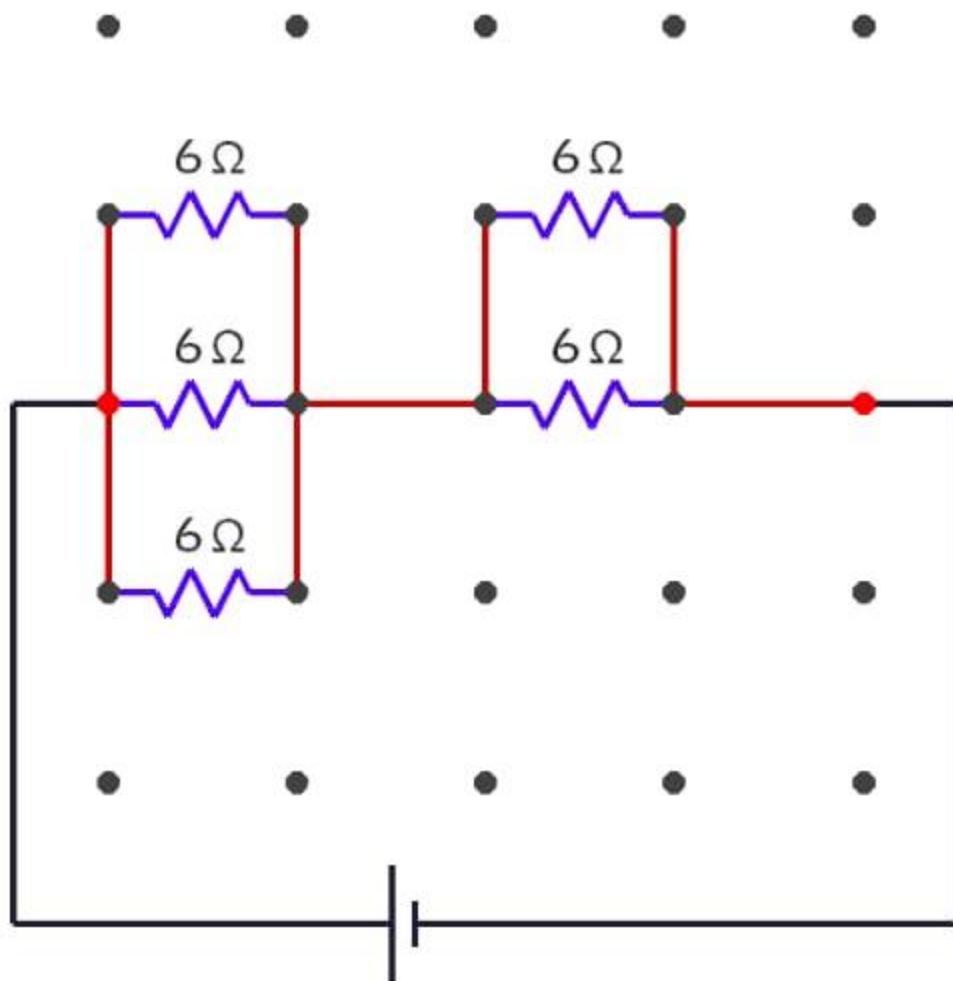
## Level Five

Connect 5 resistances (6 ohms each) in a circuit to get an equivalent resistance of 5 ohms.





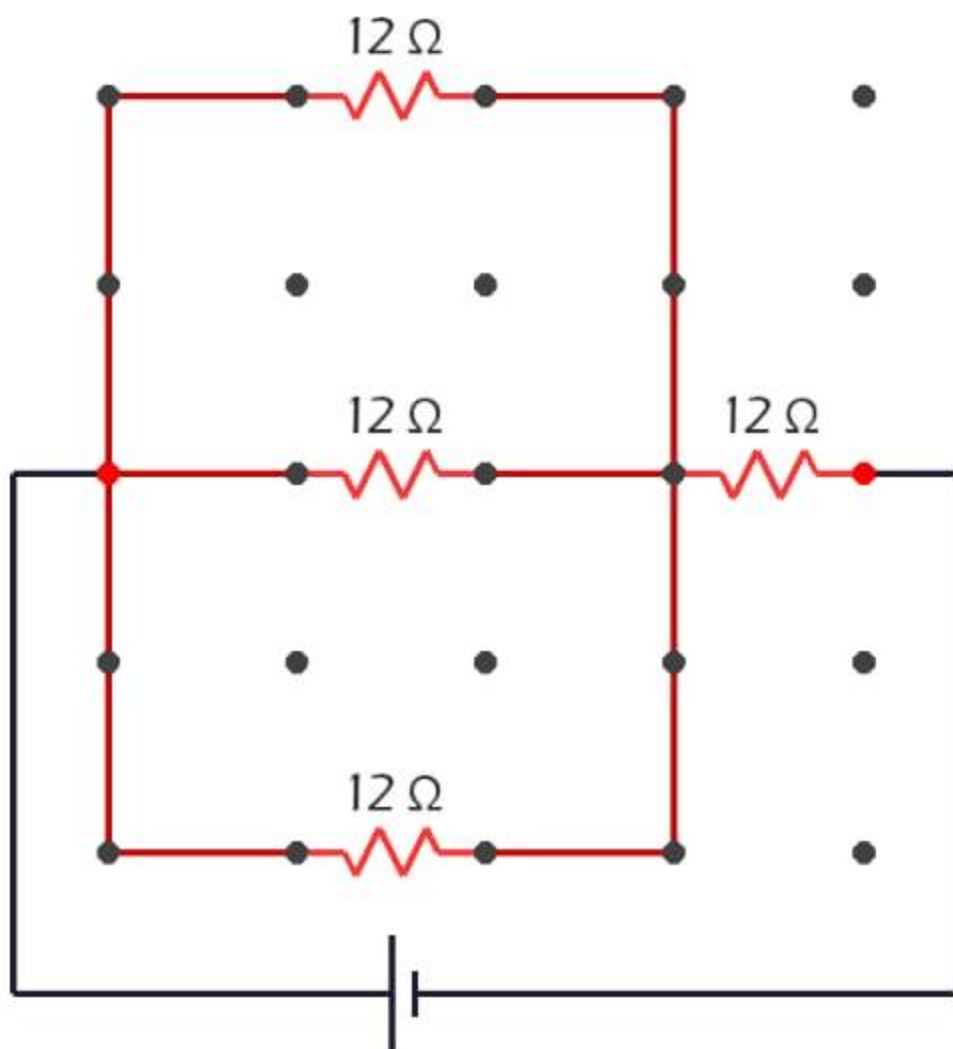Connect some more resistances (of 12 ohms each) and make a circuit with an equivalent resistance of 16 ohms.




1:50 AM

5G
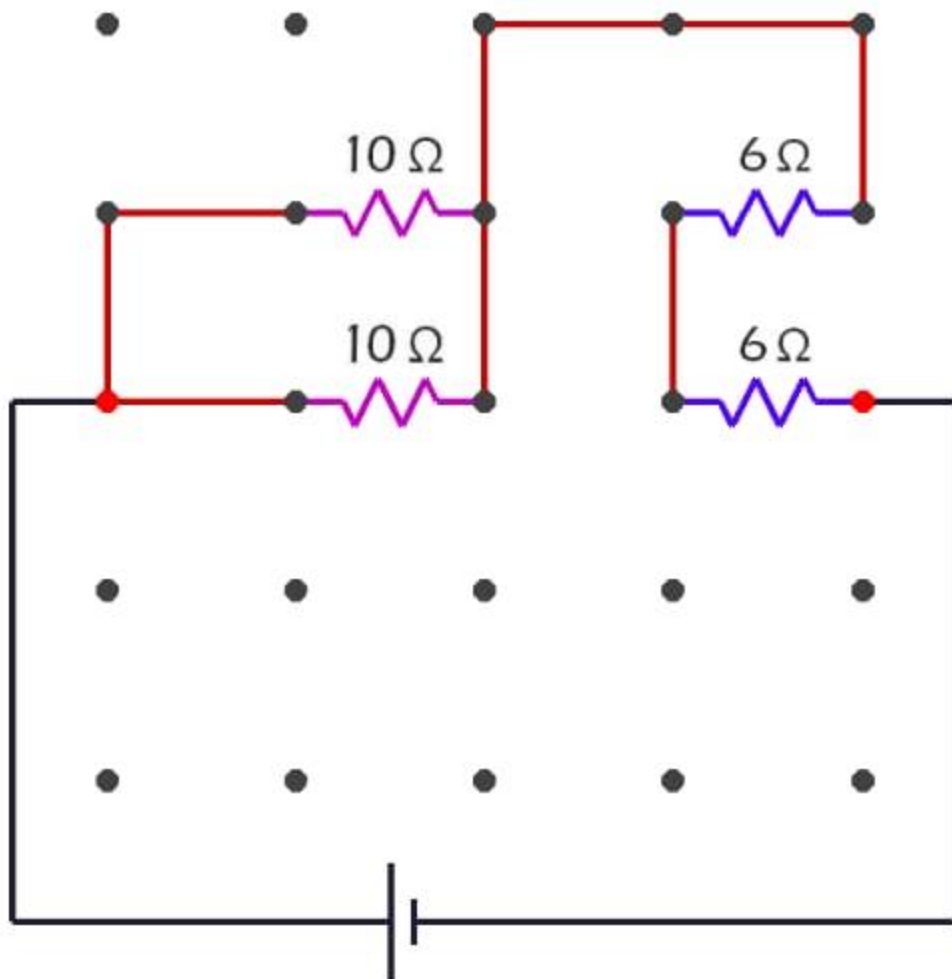
## Level Eight

Connect the given resistances to make a circuit with an equivalent resistance of 17 ohms.




8:36 PM

45%
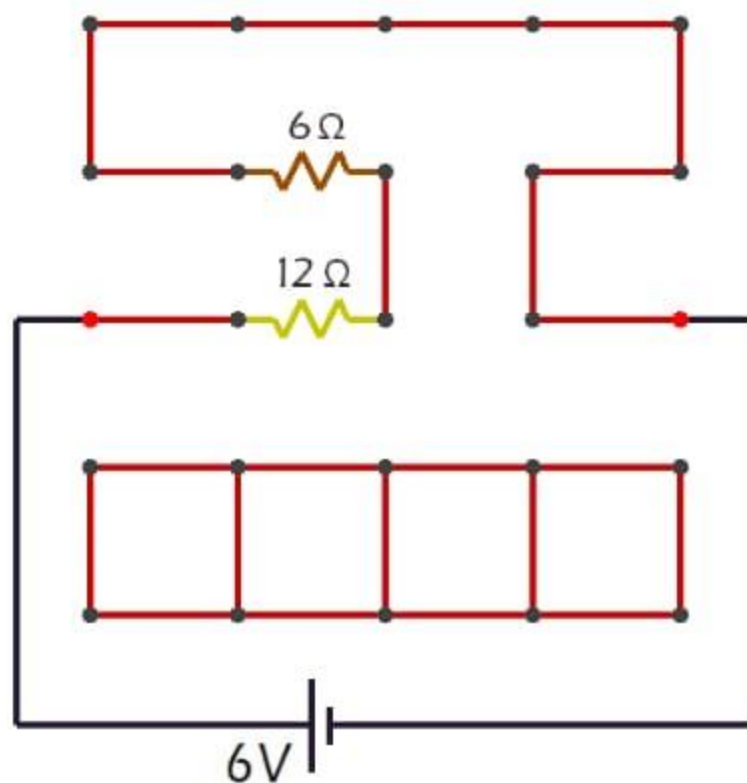
## Level Ten

Connect the given resistances in series and find the voltage drop across the 12 ohm resistance.



Answer (in volts) =

4

DONE!

BACK

1

2

3


-

3:17 PM

53%
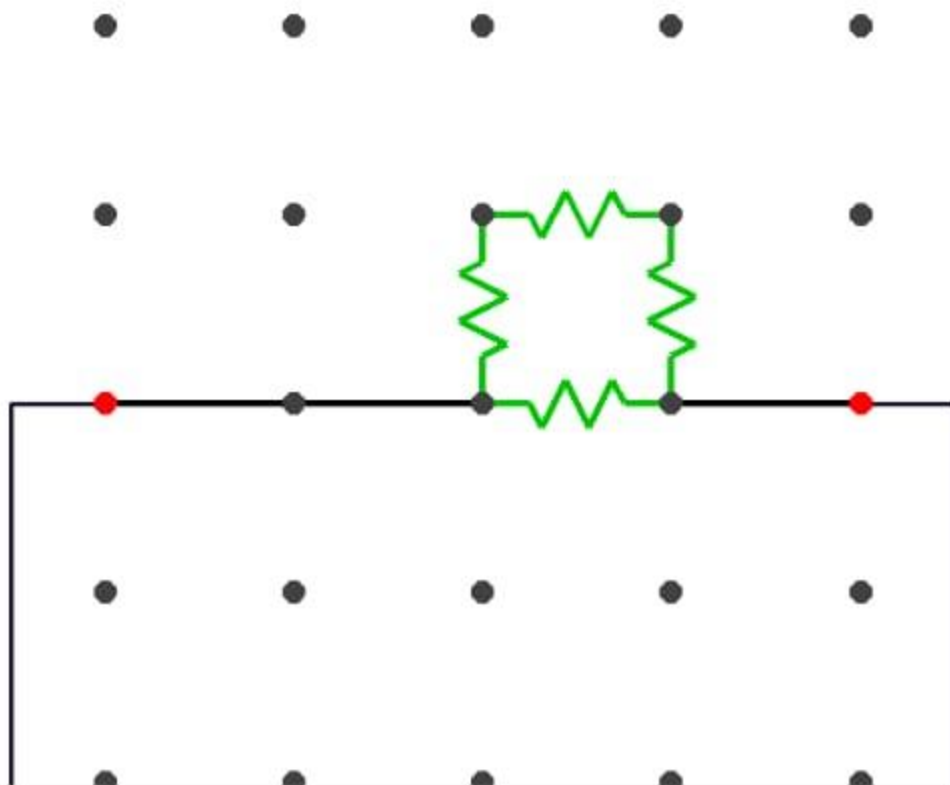
## Level Ten

All the resistances are of 12 ohms. Find the equivalent resistance of the circuit.



Equivalent resistance  
(in ohms) =

9

DONE!

BACK

1

2


3

-


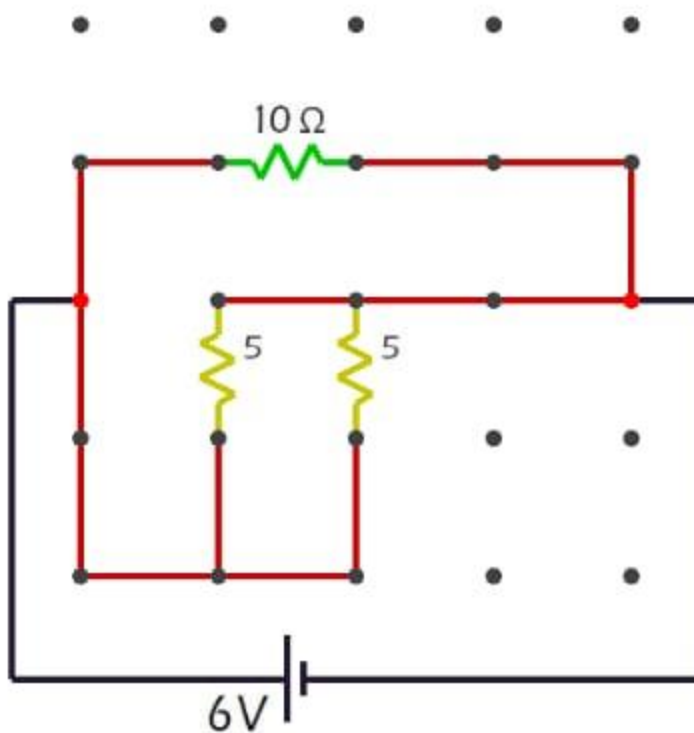
## Level Eleven

The green resistance is of 10 ohms and the yellow ones are of 5 ohms each. Connect all of them in parallel and find the current through the circuit.



Answer (in amperes) =

3

DONE!

BACK

1

2

3


-

5:18 PM

5:18 PM
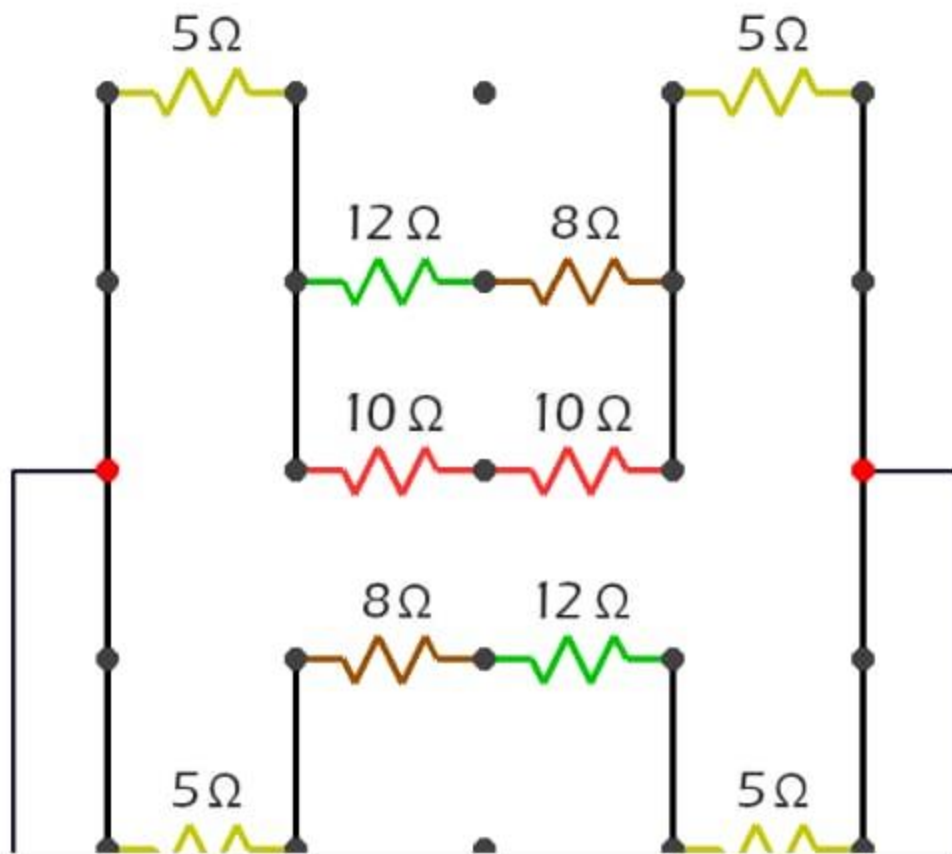
## Level Twelve

The resistances (in ohms) are as mentioned.  
Find the equivalent resistance of the circuit.



Equivalent resistance  
(in ohms) =

12

DONE!

BACK

1

2

3


-

8:44 PM

44%
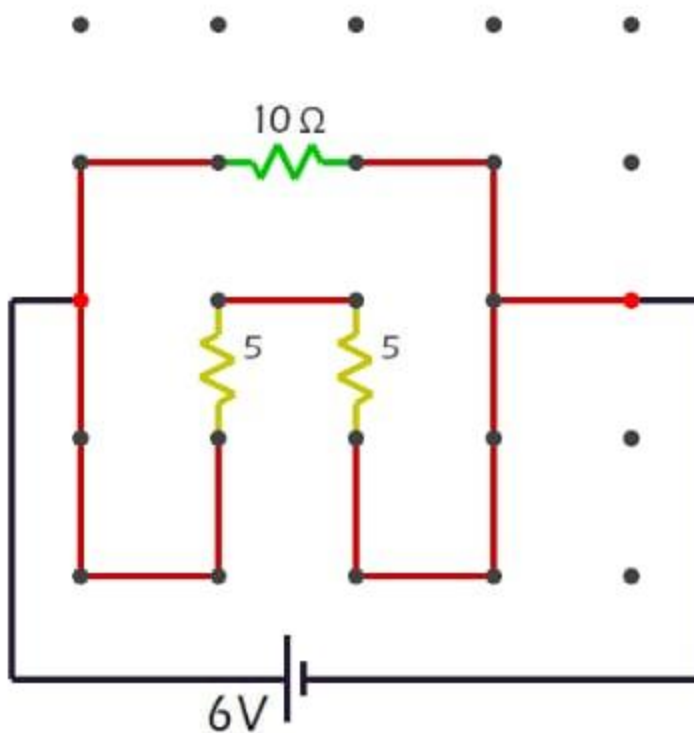
## Level Thirteen

Connect the two 5 ohm resistances in series and the 10 ohm resistance in parallel with them. Now find the current through each 5 ohm resistance.



Answer (in amperes) =

0.6

DONE!

BACK

1


2

3

-
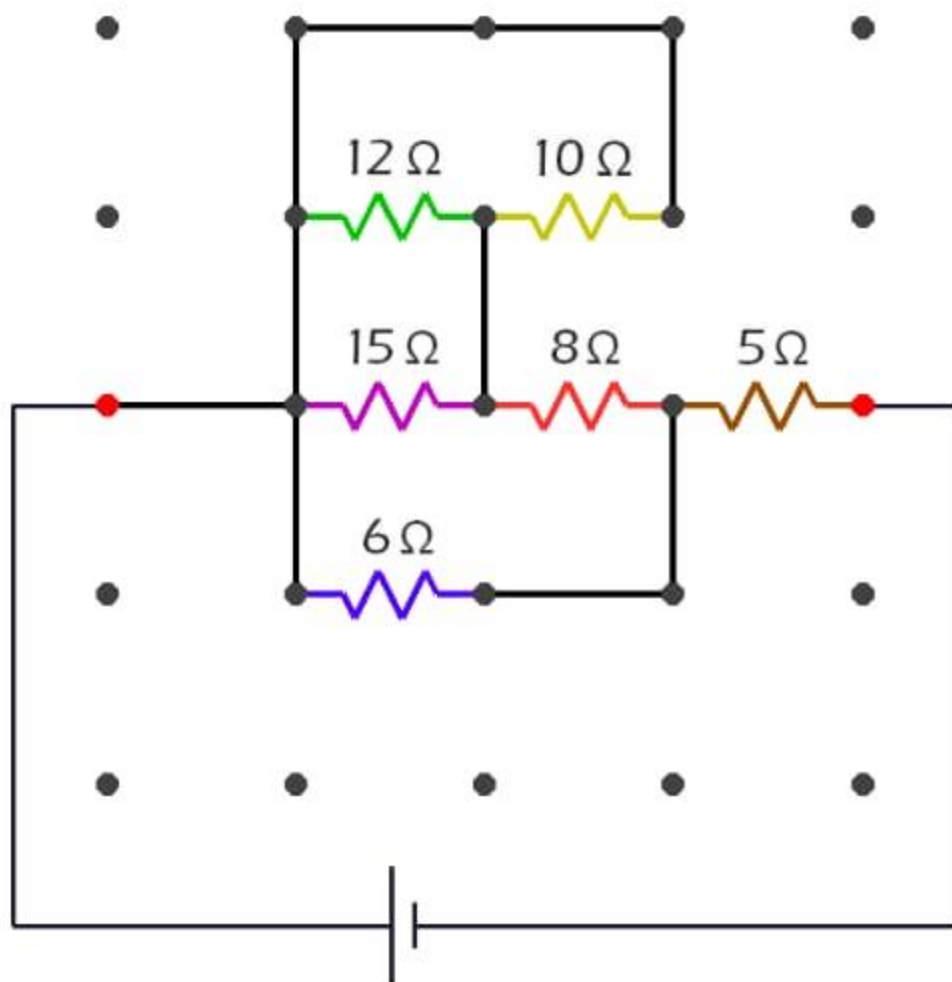
## Level Fifteen

The resistances (in ohms) are as mentioned.  
Find the equivalent resistance of the circuit.



Sir I forgot to take some of the ss so here are the taken ones.