

BE LAB TASK # 01

NAME: SHAHMEER KHAN.

STUDENT ID: 12113.

TOPIC: SAFETY MEASURE.

Calculations:

1, Current and Voltage Measuring in 2nd Circuit;

***First Current Measuring:**

Data:

$$I=??$$

$$V=12\text{v.}$$

$$R=1\text{k(ohm)}=1000\text{ ohm.}$$

Solution:

$$V=I \times R$$

$$I=V/R$$

$$I=12 / 1000.$$

$$I=0.012\text{ A.}$$

Or;

$$I=12\text{ mA.}$$

***Now for Volt Measuring:**

Data:

$$I=12\text{mA.}$$

$$V=??.$$

$$R=1\text{k}(\text{ohm})=1000 \text{ ohm.}$$

Solution:

$$V=I \times R$$

$$V=12 \times 1000 \text{ ohm} \quad \text{Or} \quad V=12 \times 1\text{k} (\text{ohm})$$

$$V=12000 \text{ mv.} \quad \text{Or} \quad V=12 \text{ v.}$$

2, Voltage Measuring in 3rd Circuit;

Data:

$$I=12\text{mA.}$$

$$V=??.$$

$$R=1\text{k}(\text{ohm})=1000 \text{ ohm.}$$

Solution:

$$V=I \times R$$


$$V=12 \times 1000 \text{ ohm} \quad \text{Or} \quad V=12 \times 1\text{k} (\text{ohm})$$

$$V=12000 \text{ mv.} \quad \text{Or} \quad V=12 \text{ v.}$$


Screen shot:

SHAHMEER (12113).


Resistance

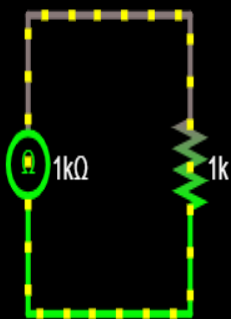

Current

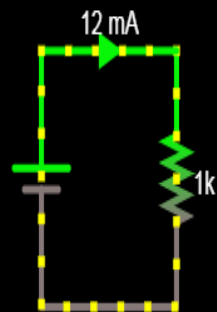

Voltage

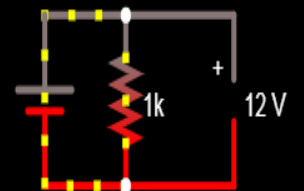

$t = 5.694\text{ s}$
time step = $5\text{ }\mu\text{s}$

Link:

<https://tinyurl.com/yyhwd6q5>
