

BE (Mid-Term Exam).

Name: Shahmeer Khan

Class ID: 106228.


Student ID: 12115.

Question no. 1) Part a)

Answer: Importance of Thevenin's Theorem:

- 1) With Thevenin Theorem, if Circuit contains multiple series and parallel connected components, including voltage and/or current sources and resistors, which will ^(Thevenin Theorem) determine the current flowing and voltage level at a point in the circuit, ^{with other method it} can be difficult and complex.
 - 2) Thevenin's Theorem is also important in such a way that, if the current is flowing at a point in a circuit, it can be calculated without knowing voltage at intermediate points in the circuit.
 - 3) Thevenin's Theorem is sometimes used in conjunction with Norton's Theorem, which is the "current source in parallel with a single resistor" equivalent.
- ① Norton's Theorem:
- "Any linear circuit containing several energy sources and resistances can be replaced by a single Constant Current generator in parallel with a single Resistor."

Question no. 1; part b;

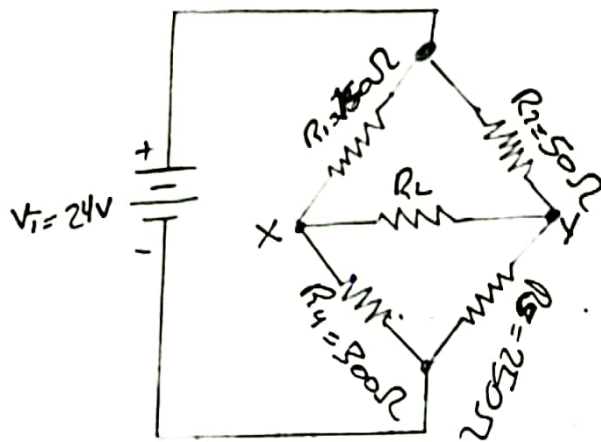

Solution:

$$\odot R_T = \left(\frac{1}{R_{14}} + \frac{1}{R_{25}} \right)^{-1}$$

$$R_T = \left(\frac{1}{R_1 + R_4} + \frac{1}{R_2 + R_3} \right)^{-1}$$

$$\therefore R_{14} = R_1 + R_4$$

$$R_{25} = R_2 + R_3$$

$$R_T = \left(\frac{1}{130 + 300} + \frac{1}{50 + 250} \right)^{-1}$$

$$R_T = \left(\frac{1}{430} + \frac{1}{300} \right)^{-1}$$

$$R_T = \left(\frac{73}{12900} \right)^{-1}$$

$$R_T = 180 \Omega \quad (\text{Total Resistance of circuit})$$

$$\odot \underline{I_T} = V_T / R_T$$

$$= \frac{24}{180}$$

$$\underline{I_T} = 0.14(A) \text{ (amp.)} \quad (\text{Total current of circuit})$$

Now voltage through R_2 :


$$V_{R_2} = \frac{R_2}{R_2 + R_5} \times V_T$$

$$\Rightarrow \frac{50}{50 + 250} \times (24)$$

$$\Rightarrow \frac{1200}{300}$$

$$V_{R_2} = 4V \quad (\text{Voltage across } R_2)$$

① Thevenin voltage $= V_{TH} = V_{R_2}$.

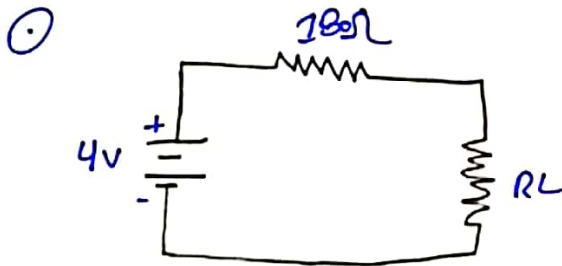

③ $R_L = 100\Omega$ (i)

$$R_T = 100 + 180$$

$$R_T = 280\Omega$$

④ $I_T = 4/280$

$$I_T = 0.014A$$

∴ Since it is a series circuit so $I_L = I_T$.

$$V = \frac{R_L}{R_T} \times V_T$$

$$V_L = \frac{100}{280} \times 4$$

$$V_L = 1.428V_L$$

Now,

(on next page)

$$\odot R_L = 200 \Omega \quad (ii)$$

$$R_T = 200 + 180$$

$$R_T = 380 \Omega$$

$$I_T = 4/380$$

$$I_T = 0.0105 A$$

\therefore Since it is series circuit so;

$$I_L = I_T$$

$$\odot V_L = \frac{200}{380} \times 4$$


$$V_L = 2.105 V$$

Shahmeer Khan.

ID: 106228


Roll ID: 12113.

Question no. 5.

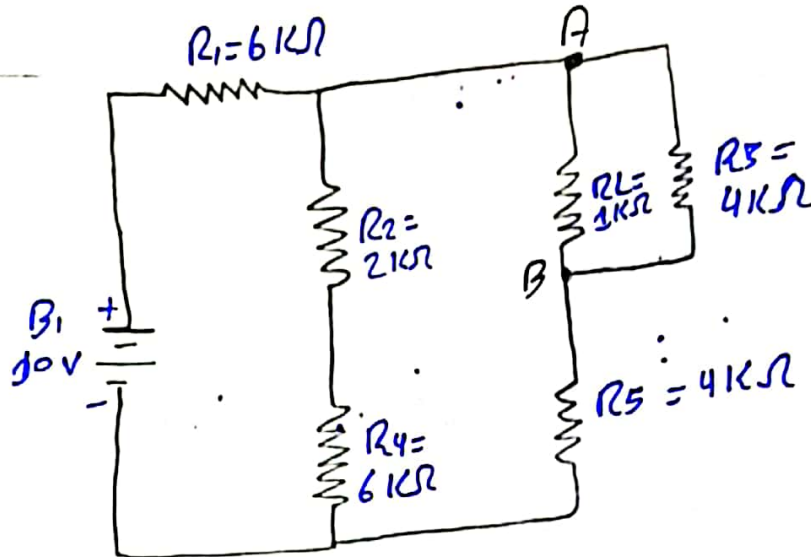

Solution:

① (Shorting A-B)

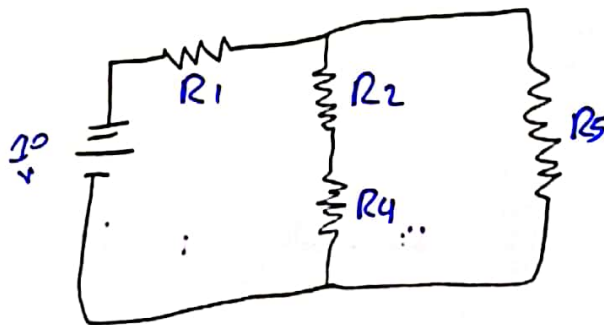

$$\begin{aligned} \textcircled{1} R_T &= \left(\frac{1}{R_2 + R_4} + \frac{1}{R_5} \right)^{-1} + R_1 \\ &= \left(\frac{1}{2000 + 6000} + \frac{1}{4000} \right)^{-1} + 6000 \end{aligned}$$

$$R_T = 8666.7 \Omega$$

$$\textcircled{2} I = V/R$$

$$= 10 / 8666.7 \Omega$$

$$I = 1.153 \times 10^{-3} \text{ amp}$$

$$\odot I_{R5} = \frac{4000}{8666.7} \times 1.155 \times 10^{-3}$$

$$I_{R5} = 5.32 \times 10^{-4} \text{ amp}$$

OR

$$I_{R5} = 0.000532 \text{ amp}$$


⊙ Opening point A-B.

$$R_T = \left(\frac{1}{2000 + 6000} + \frac{1}{4000 + 4000} \right) + R_1$$

$$R_T = 4000 + 6000$$

$$R_T = 10 \text{ k}\Omega \Rightarrow R_N = R_T = 10 \text{ k}\Omega$$

⊙ Circuit.

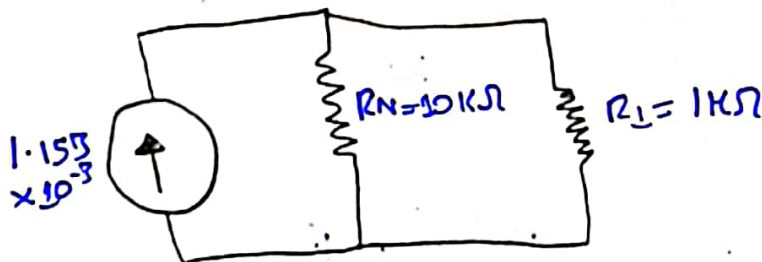

Part a)

Answer; Norton's theorem uses a current source, whereas
Thevenin's theorem uses voltage source.

Q5 Part b)

Answer

- ① Current source is the dual of voltage source.
- ② Voltage source is the combination of two terminals of like anode and cathode.


BE (Mid-Term Exam)

Name: Shahrukh Khan

Class ID: 106228

Student ID: 12117

Question no. 4:

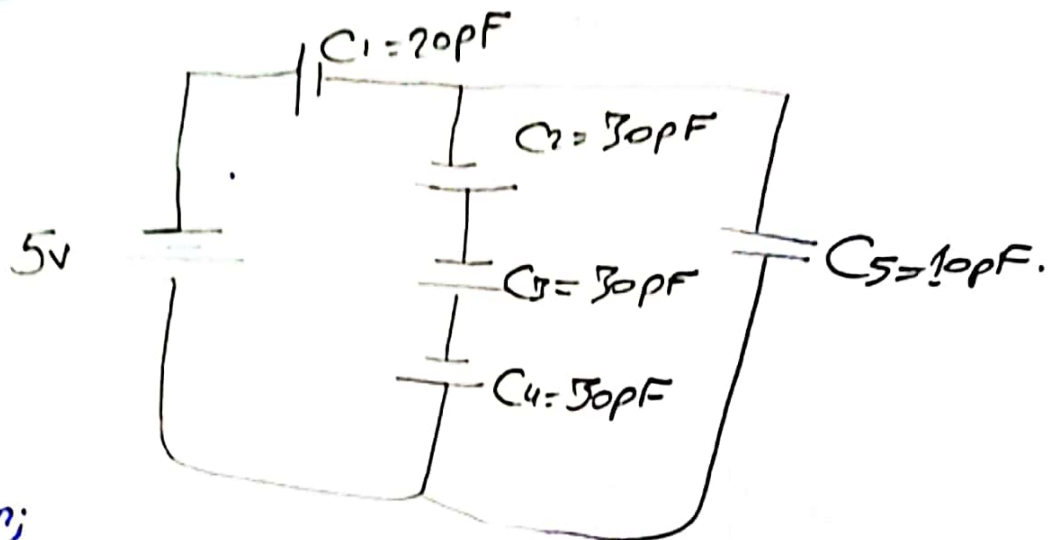

Solution:


C_1 and C_3 and C_4 are in series with each other.

$$\text{Sum of series capacitance} = C_{t1} = \left[\frac{1}{C_1} + \frac{1}{C_2} + \frac{1}{C_3} \right]^{-1}$$

$$\Rightarrow \left[\frac{1}{20} + \frac{1}{30} + \frac{1}{30} \right]^{-1}$$

$$C_{t1} = 10pF$$

Now Circuit

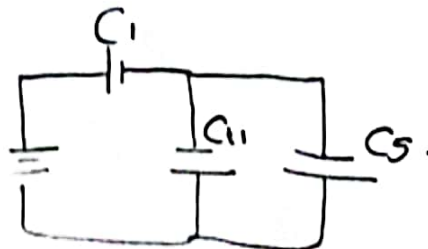


Now, $C_{t1} \parallel C_5$

$$C_{t2} = C_{t1} + C_5 \\ = 10pF + 10pF$$

$$C_{t2} = 20pF$$

① Now Circuit

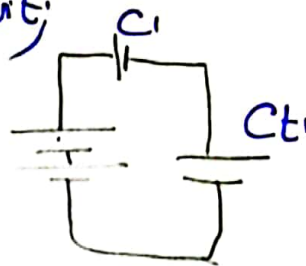

② \therefore Sum of series circuit

$$C_t = \left[\frac{1}{C_1} + \frac{1}{C_{t1}} \right]^{-1}$$

$$= \left[\frac{1}{20} + \frac{1}{20} \right]^{-1}$$

$$C_t = 10 \text{ pF}$$

③ Total Capacitance = 10 pF

or

$$C_T = 10 \times 10^{-12} \text{ F}$$

④ Total Charge (Q_T):

$$V_T = 5 \text{ V}$$

$$C_T = 10^{-12} \text{ F}$$

$$V_T = \frac{Q_T}{C_T}$$

$$\Rightarrow 5 = \frac{Q_T}{10^{-12}}$$

$$\Rightarrow Q_T = \text{Total charge} = 5 \times 10^{-12} \text{ coulomb (C)}$$

Question no 5; Part 1;

Part a;

a) $\theta = \frac{5\pi}{4}$

Solution;

$\odot \rightarrow$ degree;

$$\text{degree} = \left(\frac{180^\circ}{\pi} \right) \times \text{rad.}$$

$$\text{degree} = \left(\frac{180^\circ}{\pi} \right) \times \left(\frac{5\pi}{4} \right)$$

$$\boxed{\text{degree} = 225^\circ}$$

Now;

$$V = V_m \sin \theta$$

$$V = 540 \times \sin 225^\circ$$

$$\boxed{V = -240.41}$$

Part b;

b) $\theta = \frac{\pi}{4}$,

Solution;

\rightarrow degree;

$$\text{degree} = \left(\frac{180^\circ}{\pi} \right) \times \left(\frac{\pi}{4} \right)$$

$$\boxed{\text{degree} = 45^\circ}$$

Now;

$$V = V_m \sin \theta$$

$$V = 540 \times \sin 45^\circ$$

$$\boxed{V = 240.41}$$

Part c;

$$c) \theta = \frac{3\pi}{2}$$

Solution;

→ degree;

$$\text{degree} = \left(\frac{180^\circ}{\pi} \right) \times \text{rad.}$$

$$\text{degree} = \left(\frac{180^\circ}{\pi} \right) \times \left(\frac{3\pi}{2} \right)$$

$$\text{degree} = 270^\circ$$

Now;

$$V = V_m \sin \theta$$

$$V = 570 \times \sin 270^\circ$$

$$V = -570$$

Question no 6; (May 1)

1) Answer;

It can be possible with the overall circuit resistance may be too high. The more the resistance will be the more the ~~current~~ battery will deliver charges causing it to drain faster.

2) Answer;

For higher power electric circuits more energy is required. AC can be transmitted with much lower energy loss as compared to DC and alternating AC is easier.

3) Answer;

Some charges repels in the capacitors which slows the flow as the capacitor is charged. When the capacitor is fully charged, the current decreases till 0.

4) Answer;

Current (I) can pass through the conductor which generates an electric field, which cuts the uniform magnetic field, inducing current on the coil.

Question no. 2;

Solution;

By Applying KCL;

$$V_1 = 10V$$

$$\frac{V_2 - V_1}{2} + \frac{V_2 - V_3}{2.5} + \frac{V_2 - V}{4} = 0$$

$$\Rightarrow \frac{5V_2 - 5V_1 + 4V_2 - 4V_3 + 2.5V_2 - 2.5V}{10} = 0$$

$$\Rightarrow 11.5V_2 - 5V_1 - 4V_3 = 0 \text{ ---- (eq. 1)}$$

$$4V = V_3$$

\Rightarrow