

BE LAB TASK # 05

NAME: SHAHMEER KHAN.

STUDENT ID: 12113.

CLASS ID: 106293.

TOPIC: SERIES AND PARALLEL
COMBINATION CIRCUIT.

TASK:

OBSERVATION/CALCULATIONS:


Objectives:

- A, Identify series and parallel combination circuits.
- B, Measure the Current Flow in a Series Circuit using Ammeter.
- C, Find out the Current Passing through the R6, R4 and R5.
- D, Measure the voltage drop across each individual resistor using Digital Multi-meter.


On Next Page.

Objectives A:

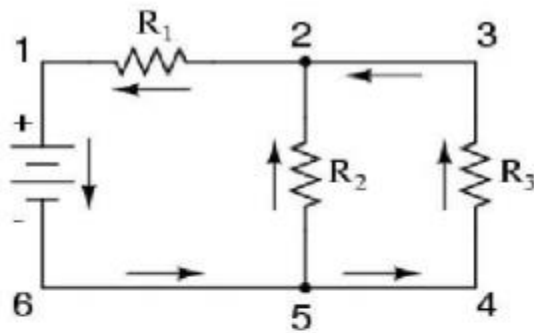
A, Identify Series and parallel combination circuit.




(a)

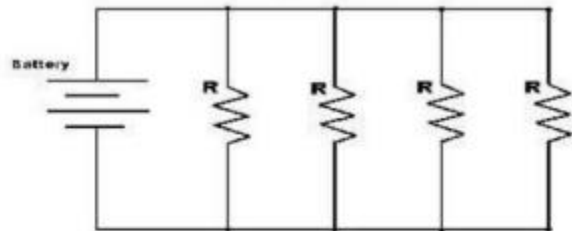

(b)

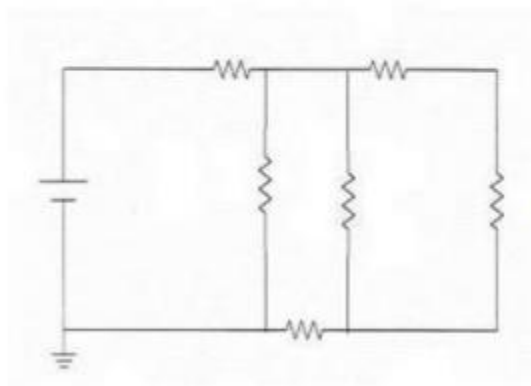

(c)

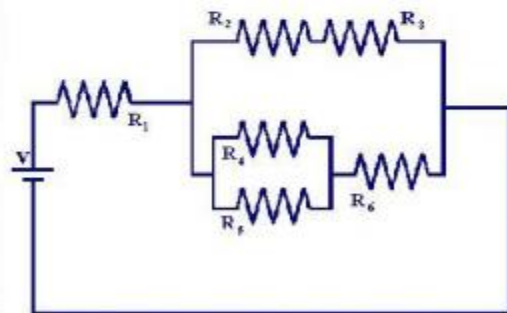

(d)

Answer: a, c, d

Objective B:

B, Measure the Current Flow in a Series Circuit using Ammeter.

- Connect the circuit shown in Fig-1. Note that the ammeter, set to the 0-100mA dc range, must be connected in series to measure the total circuit current.

$$I_T = 27.023 \text{ mA DC.}$$

- Adjust the voltage 15 V.
- You can also find total circuit resistance by Ohm's law. As you have been already told in theory class how to find the total resistance in Series-parallel circuit. Find out the total resistance of Fig shown below.

- Answer:

- **Calculating Circuit Resistance by Ohm's Law:**

- Solution:

- $V = IR$.

$$15V = (0.027023 \text{ A}) \times R$$

$$R = 555.082 \text{ Ohms.}$$

- **Total Resistance of Fig shown step by step also:**

- Solution:

1. List's Values for Resistors:

$$R_1 = 1000 \text{ Ohms.}$$

$$R_2 = 250 \text{ Ohms.}$$

$$R_3 = 250 \text{ Ohms.}$$

$$R_4 = 100 \text{ Ohms.}$$

$$R_5 = 750 \text{ Ohms.}$$

$$R_6 = 300 \text{ Ohms.}$$

2. First Considering R_1 , R_2 , R_3 for Calculations:

$$R_1 = 1000 \text{ Ohms.}$$

$$R_2 = 250 \text{ Ohms.}$$

$$R_3 = 250 \text{ Ohms.}$$

- a. Solving R_2 , R_3 first as they are in Series:

$$R_{23} = R_2 + R_3.$$

$$R_{23}=250+250.$$

$$R_{23}=500 \text{ Ohms.}$$

- b. Now solving for R_1 and R_{23} as now they are in parallel now:

$$1/R_{123}=1/R_1+R_{23}.$$

$$1/R_{123}=1/1000+1/500.$$

$$1/R_{123}=3/1000.$$

$$R_{123}=333.334 \text{ Ohms.}$$

3. Now Considering R_4 , R_5 , R_6 for Calculations:

$$R_4 = 100 \text{ Ohms.}$$

$$R_5 = 750 \text{ Ohms.}$$

$$R_6 = 300 \text{ Ohms.}$$

- a. Solving R_4 and R_5 first as they are in series:

$$R_{45}=R_4+R_5.$$

$$R_{45}=100+750.$$

$$R_{45}=850 \text{ Ohms.}$$

- b. Now solving for R_{45} and R_6 as now they are in parallel:

$$1/R_{456}=1/R_{45}+1/R_6.$$

$$1/R_{456}=1/850+1/300.$$

$$1/R_{456}=23/5100.$$

$$R_{456}=221.734 \text{ Ohms.}$$


4. Now Total Resistance of Circuit " R_T ":

*Since R_{123} and R_{456} are now in series so:

$$R_T=R_{123}+R_{456}.$$

$$R_T=333.334+221.734.$$

$$R_T=555.068 \text{ Ohms.}$$

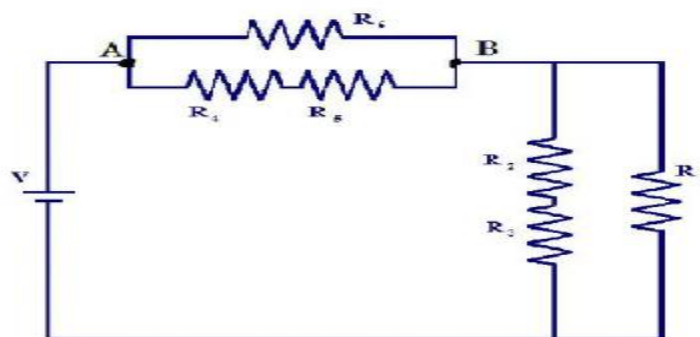

Objective C:

C, Find out the current passing through the R6, R4 and R5.

$$I_{R6-PointB} = 19.974 \text{ mA DC.}$$

$$I_{R4-R5} = 7.05 \text{ mA DC.}$$

$$I_{R5-PointB} = 7.05 \text{ mA DC.}$$

Objective D:

D, Measure the voltage drop across each individual resistor using the Digital Multi-Meter.

$$V_{R1} = 9.008 \text{ V DC.}$$

$$V_{R2} = 4.504 \text{ V DC.}$$

$$V_{R3} = 4.504 \text{ V DC.}$$

$$V_{R4} = 0.704 \text{ V DC.}$$

$$V_{R5} = 5.287 \text{ V DC.}$$

$$V_{R6} = 5.992 \text{ V DC.}$$

- Calculate the Total circuit current of above figure.

$$I_T = 27.023 \text{ mA DC.}$$

Proof:

$$V_T = I_T R_T$$


$$15 / 0.555068 = R_T$$

$$I_T = 27.023 \text{ mA DC.}$$

- Is it easy to work with series-parallel circuit together, instead of creating separate series and parallel circuit(if No, Justify)?

Answer: No, Because the calculations in Series-Parallel Circuits are complicated as compare to the separate series and parallel circuits.

Screenshot:

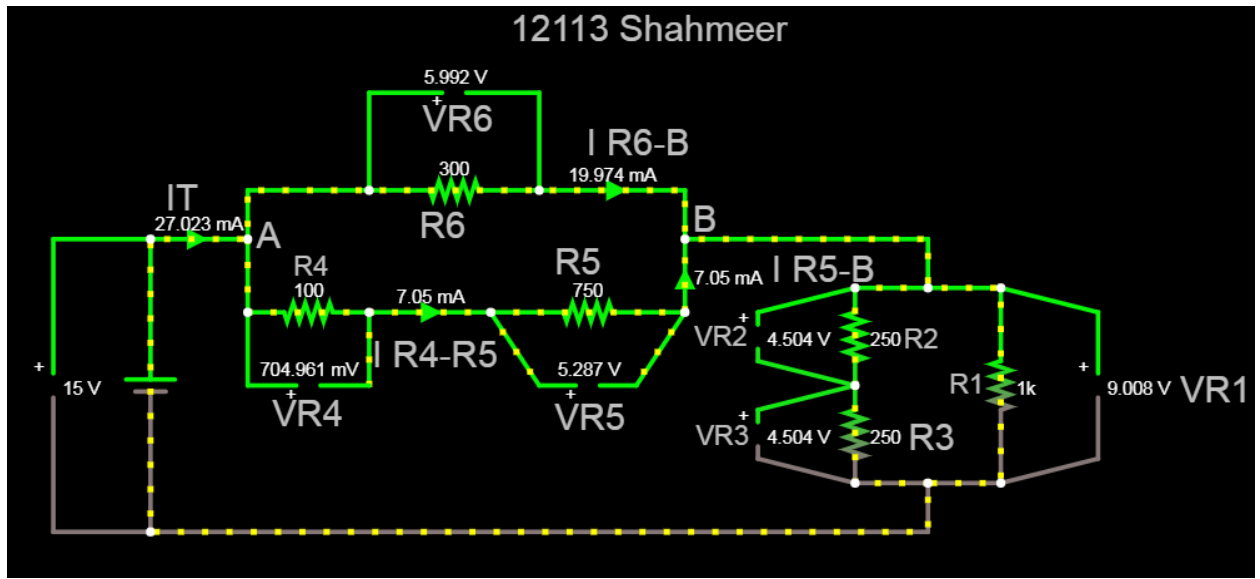

Link:

<https://tinyurl.com/y5qvd9ww>